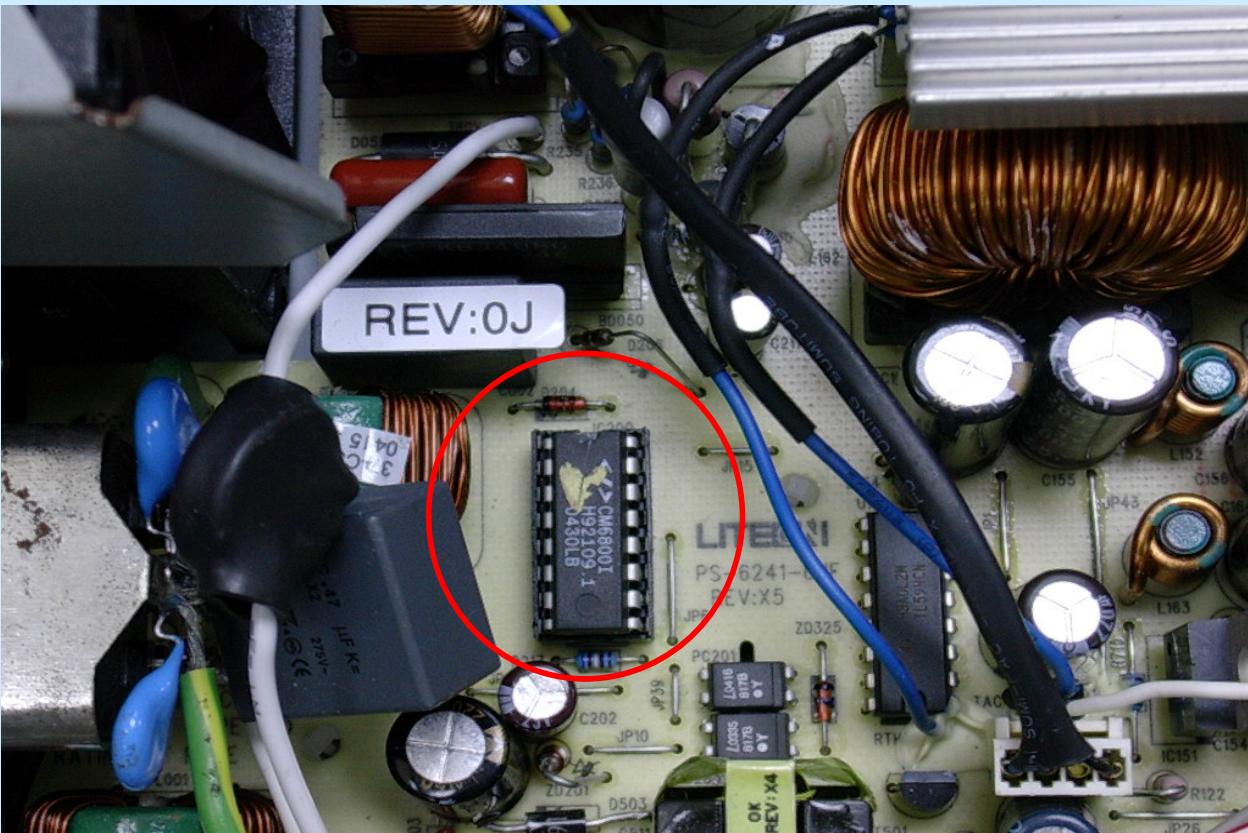


# Championmicro

## CM6800 PFC/PWM combo controller



AE/Elvis

Goal:

Input current shaping(PFC stage)

Output voltage regulation(PWM stage)

Application product:

ATX power



LCD TV

PDP

IPC

:

# Active PFC Power Supply

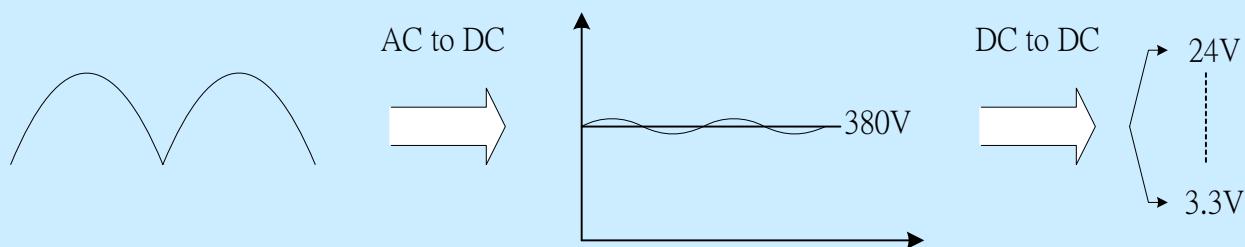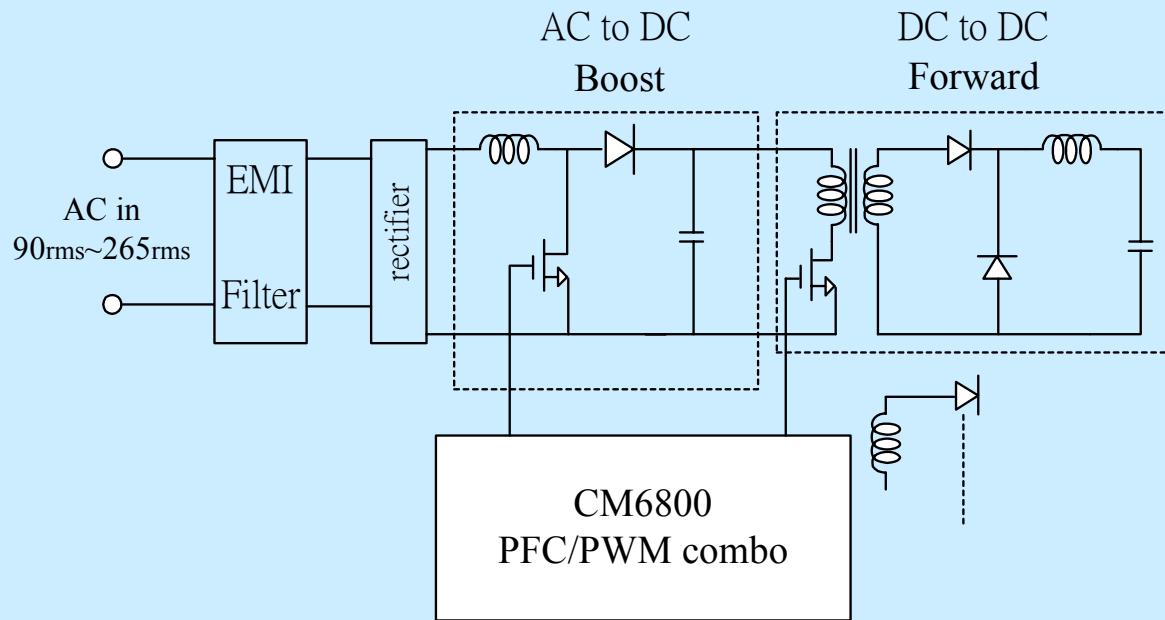

# Functions

PFC :PFC O.V.P

vin-ok (PFC/O.K)

VCC O.V.P

VCC U.V.L.O


Input current limit

PFC low power detect


PWM :Soft-start

PWM current limit

# CM6800 Block

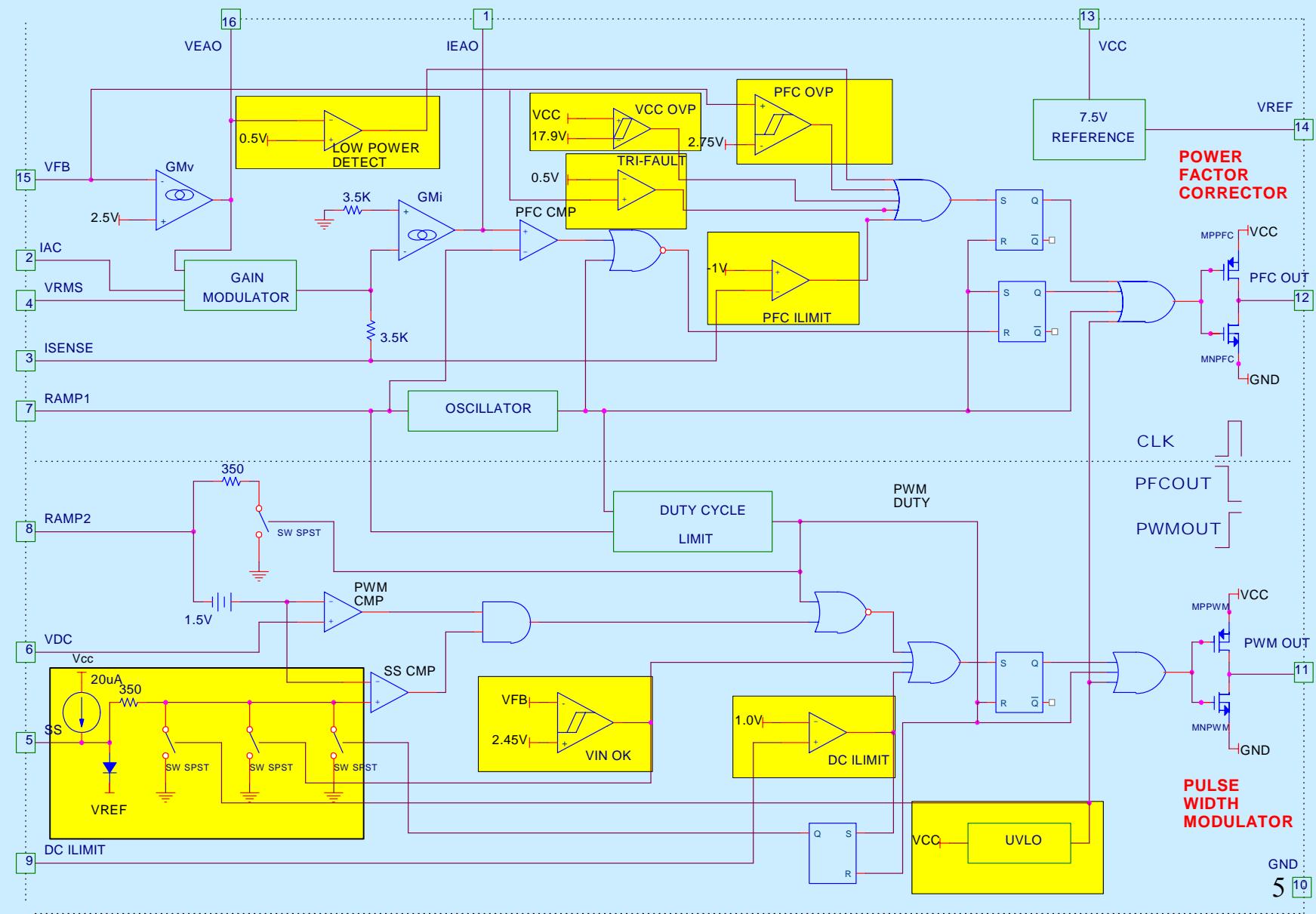


# PFC block

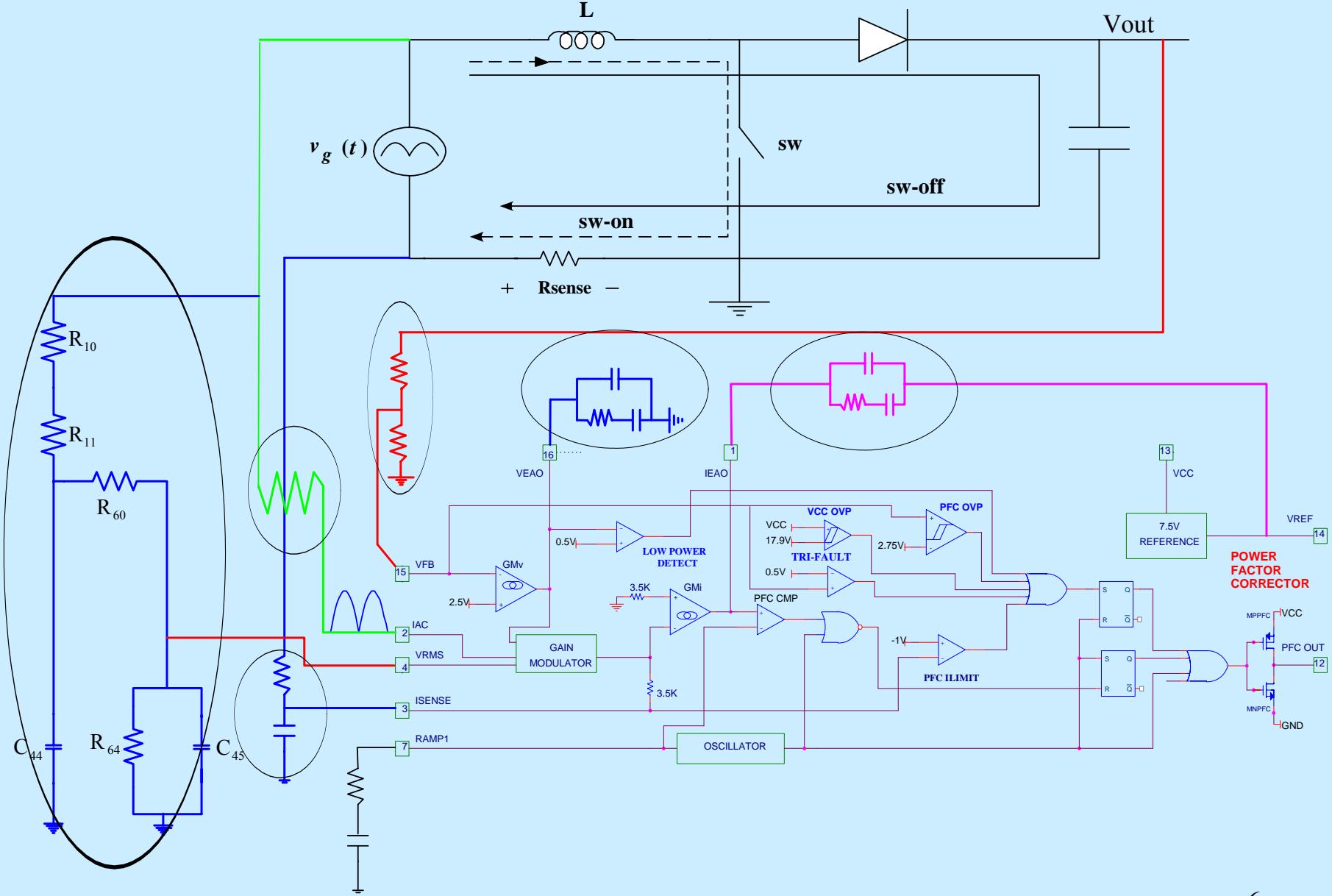

# Topics


- PFC turn-on-off
- PFC O.V.P
- VFB
- Input current limit
- PFC low power detect
- PWM turn-on-off
- PFC-PWM timing
- VCC O.V.P
- VCC U.V.L.O
- PWM current limit
- Control
- Compensation

# PFC turn-on

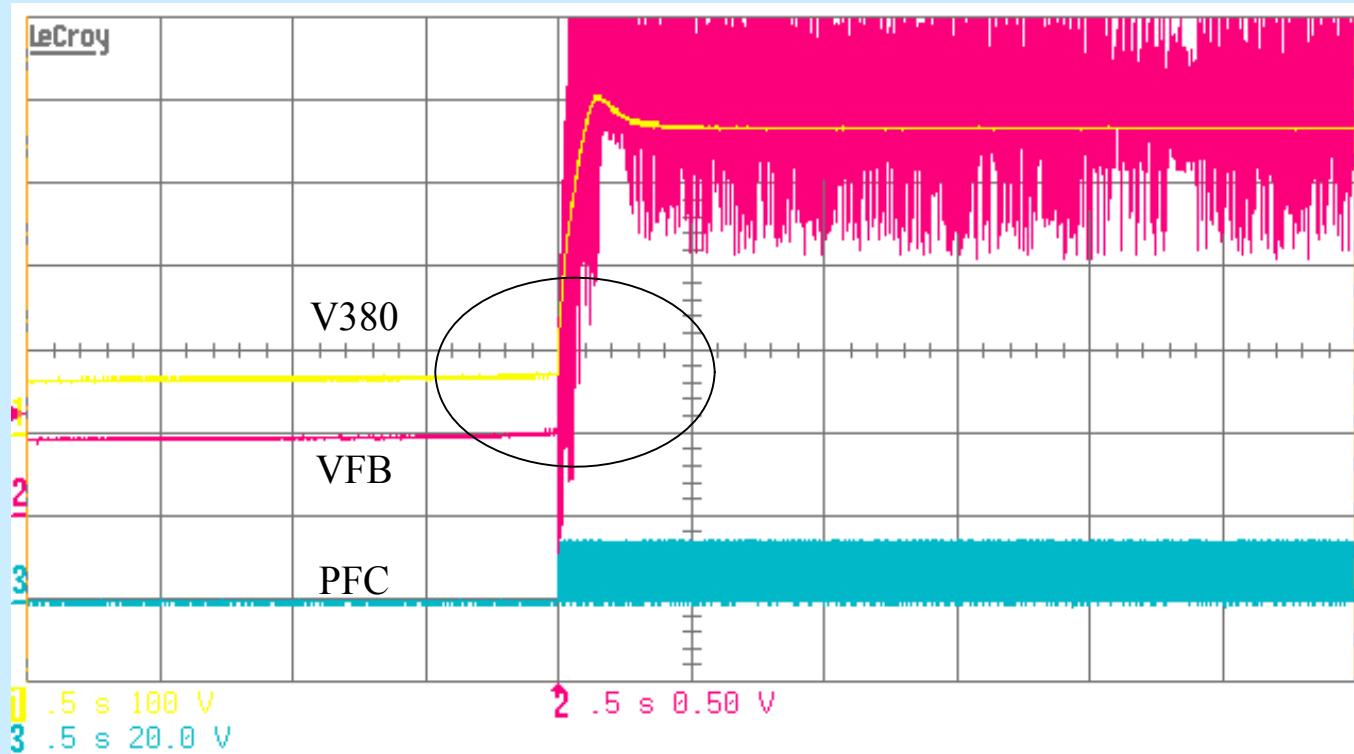


- $V_{FB} > 0.5V \rightarrow$  PFC turn-on
- $V_{FB} = 2.5V \rightarrow$  PFC stage OK (vin O.K)

# PFC turn-off

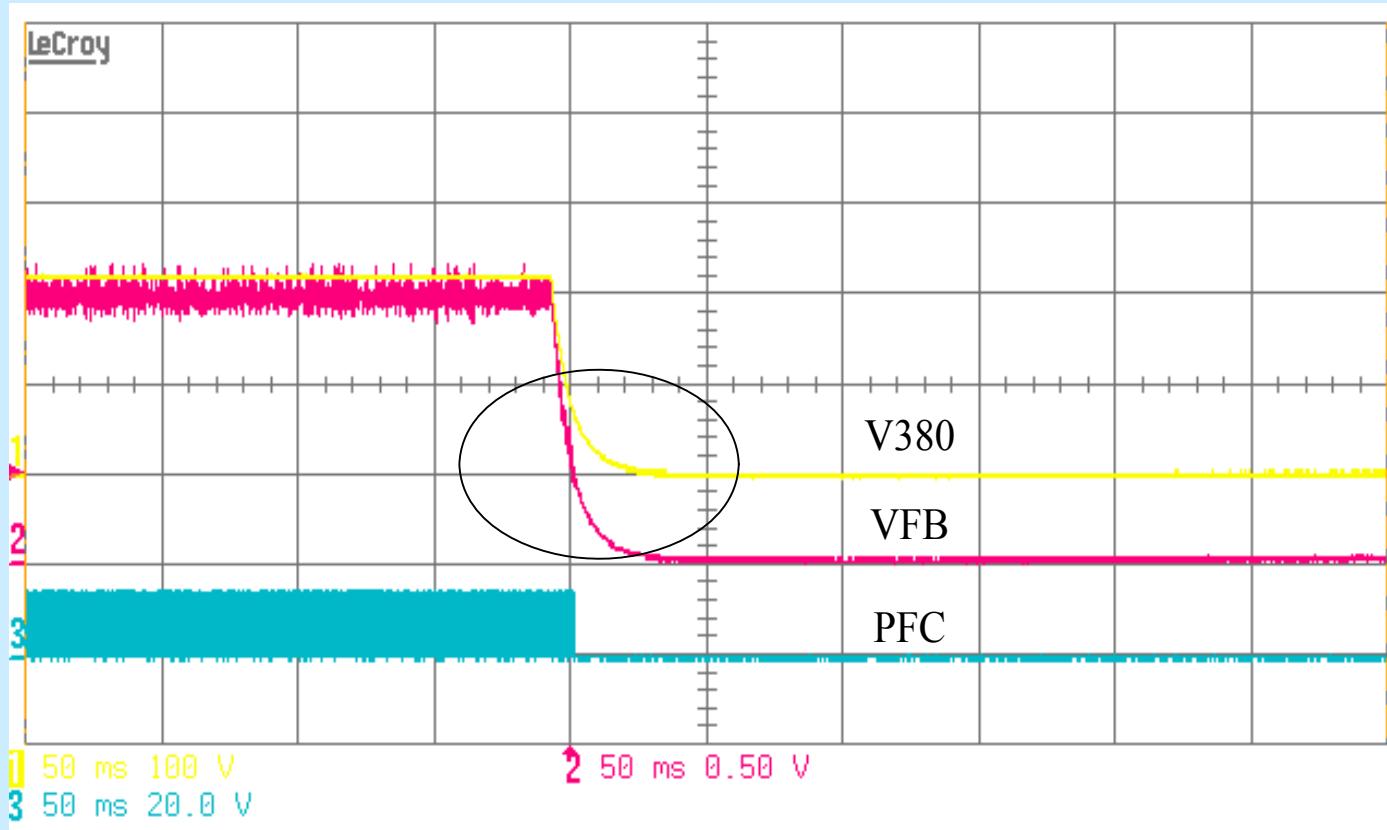


- $V_{FB} < 0.5V \rightarrow$  PFC turn-off

# PFC O.V.P

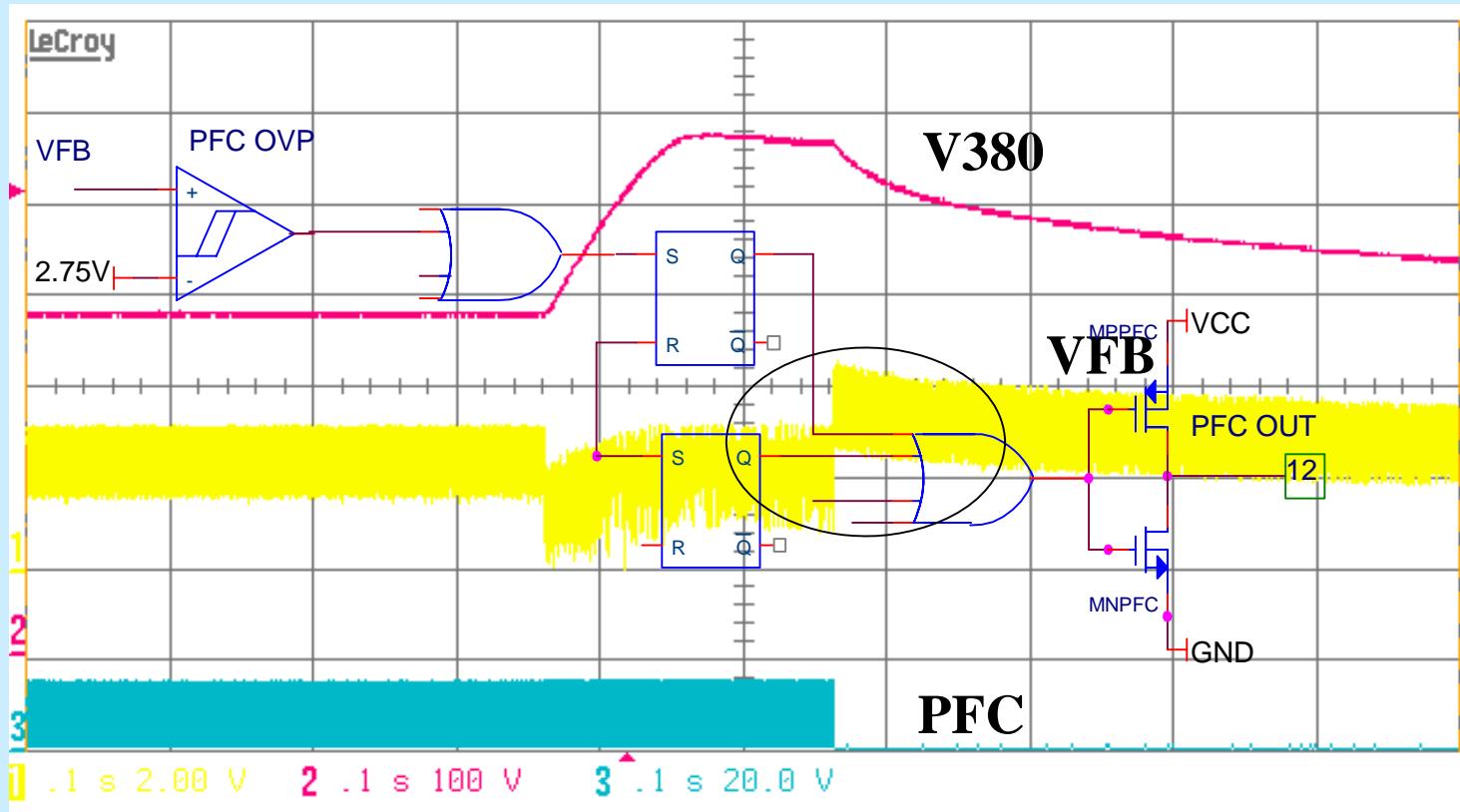


VFB>2.75V → PFC turn-off

# VFB

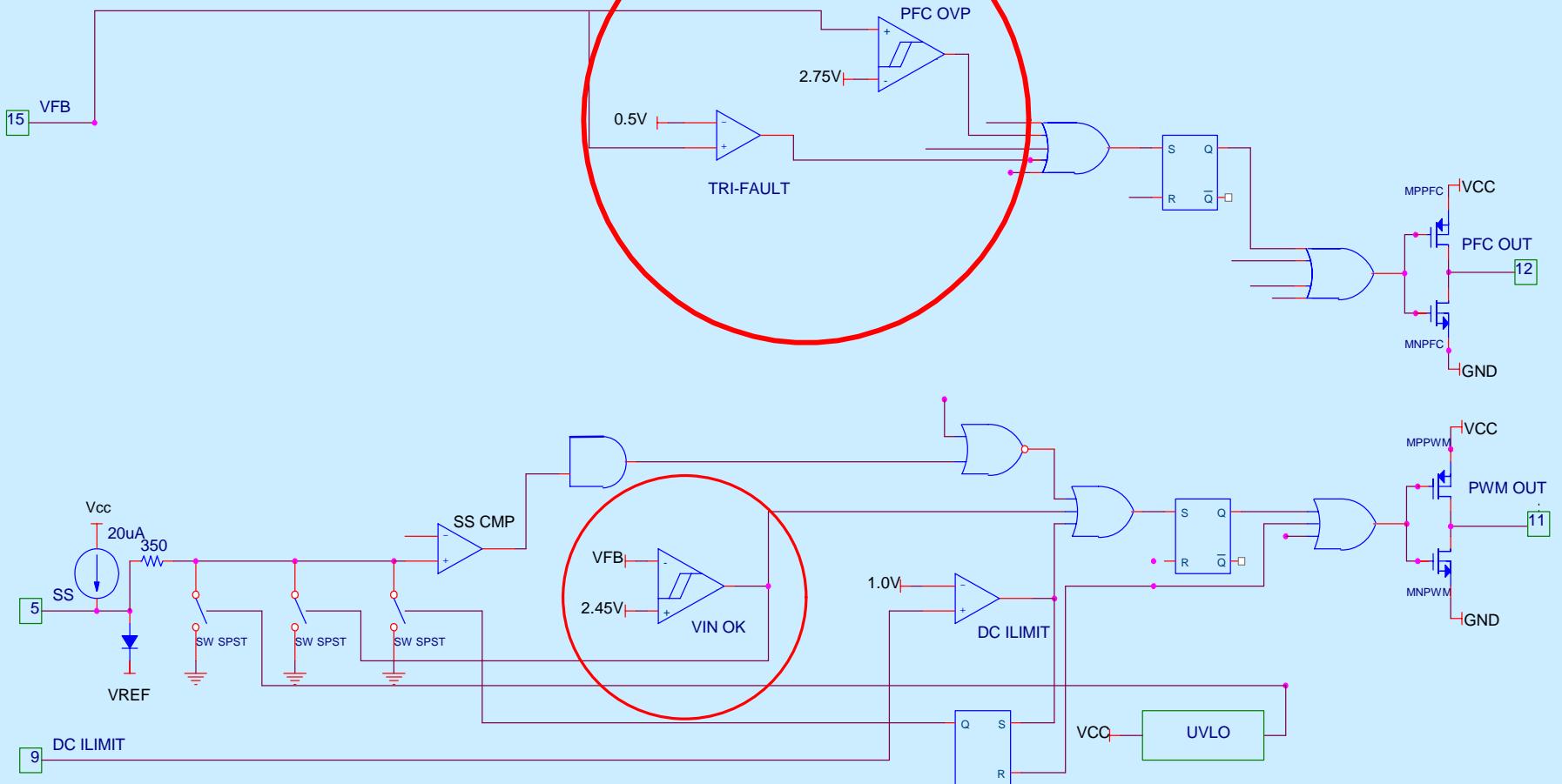


# VFB

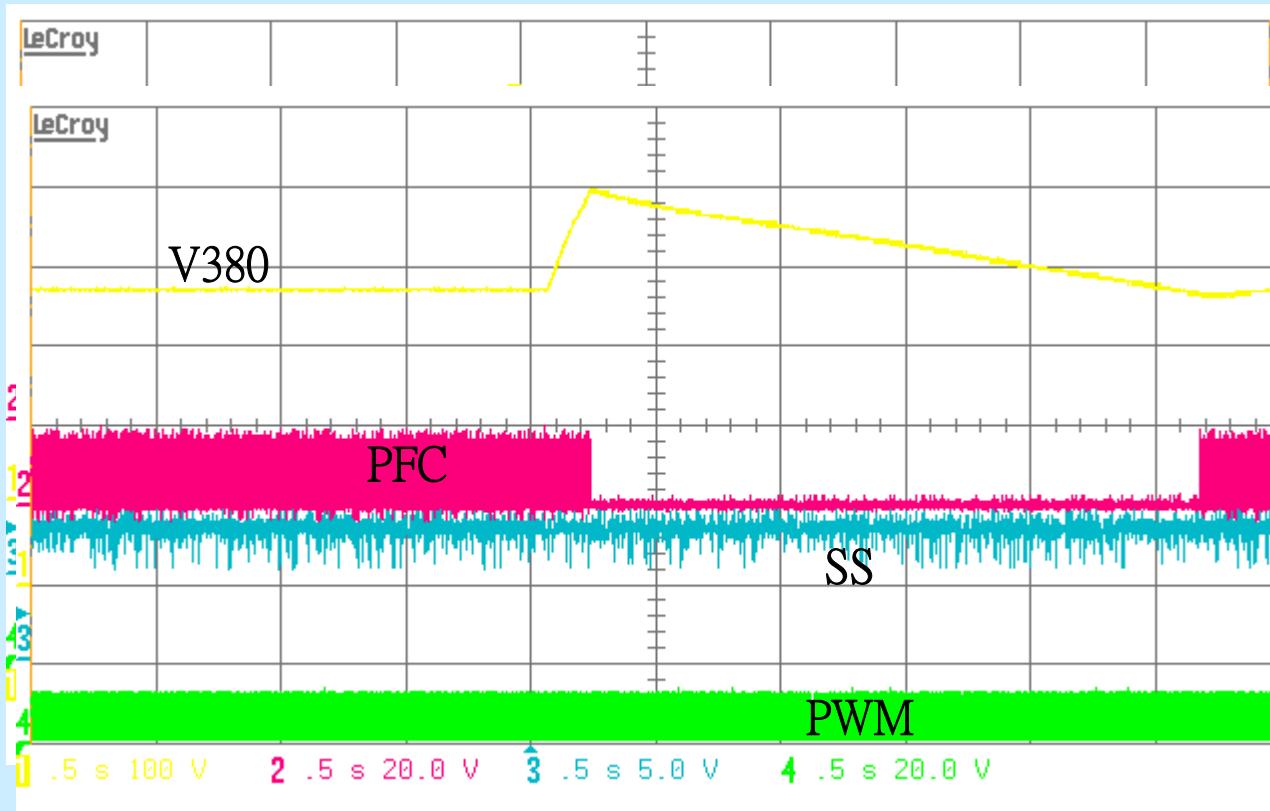


**VFB>2.75V PFC turn-off**

**VFB<2.5V PWM turn-off**

# input current limit

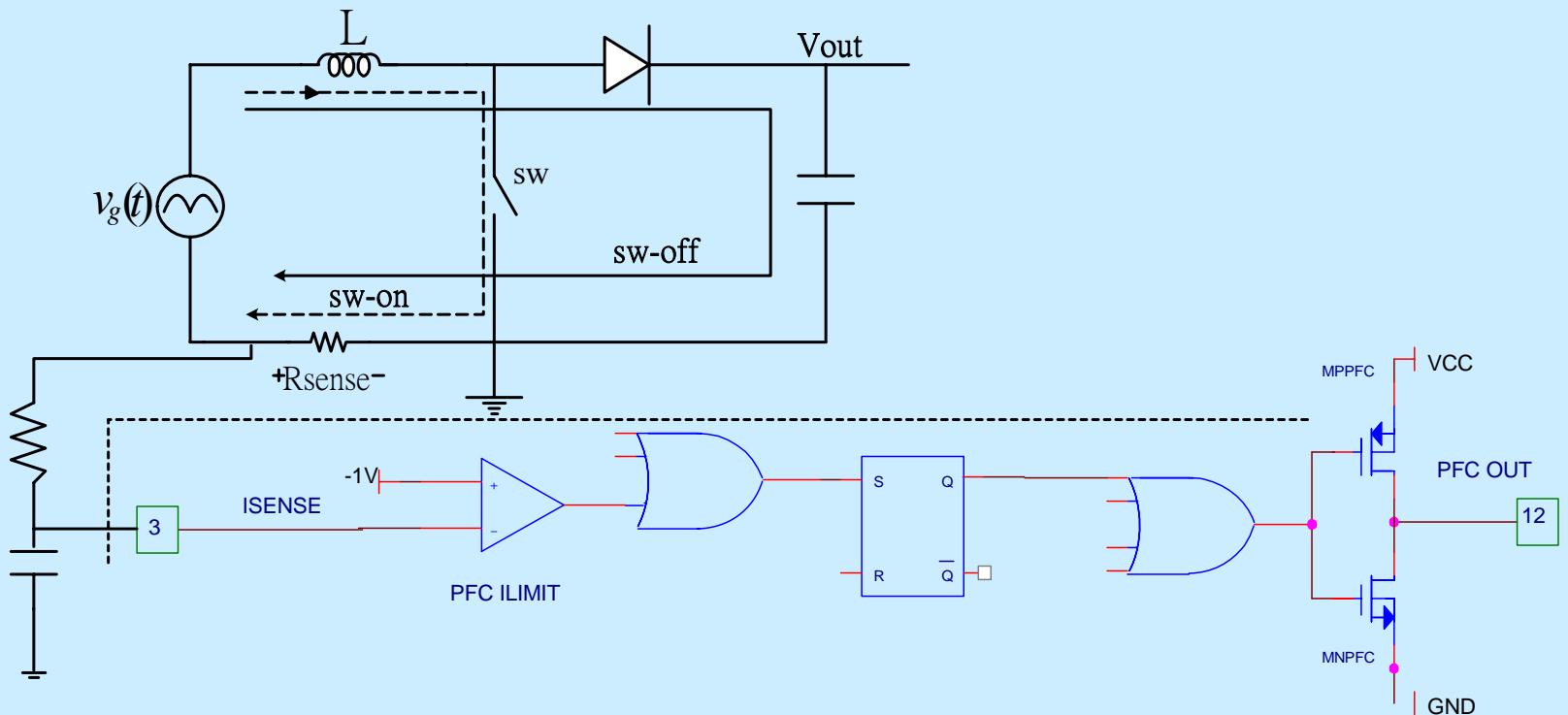


# Current waveform

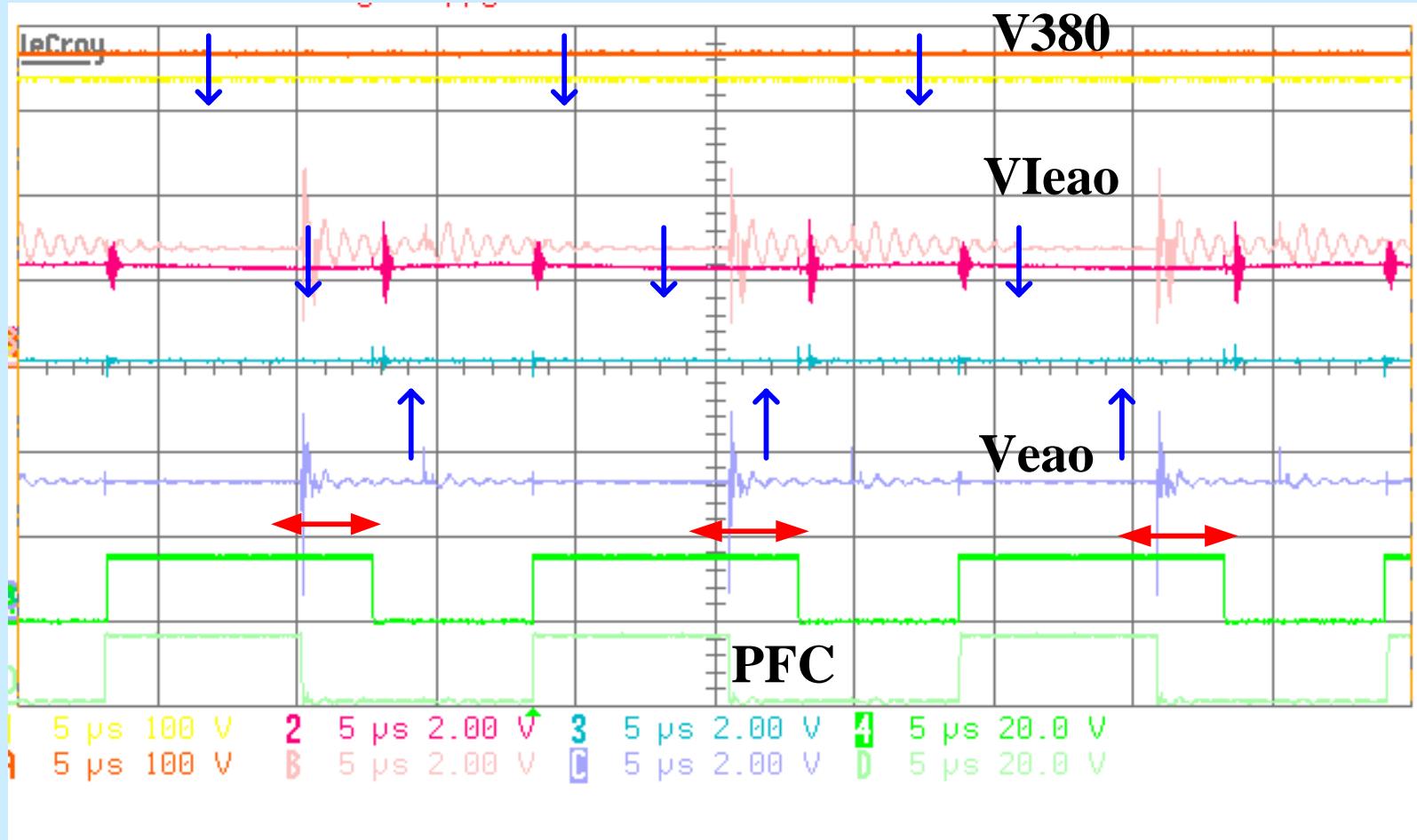


PFC duty cycle by cycle reduce

# PFC low power detect

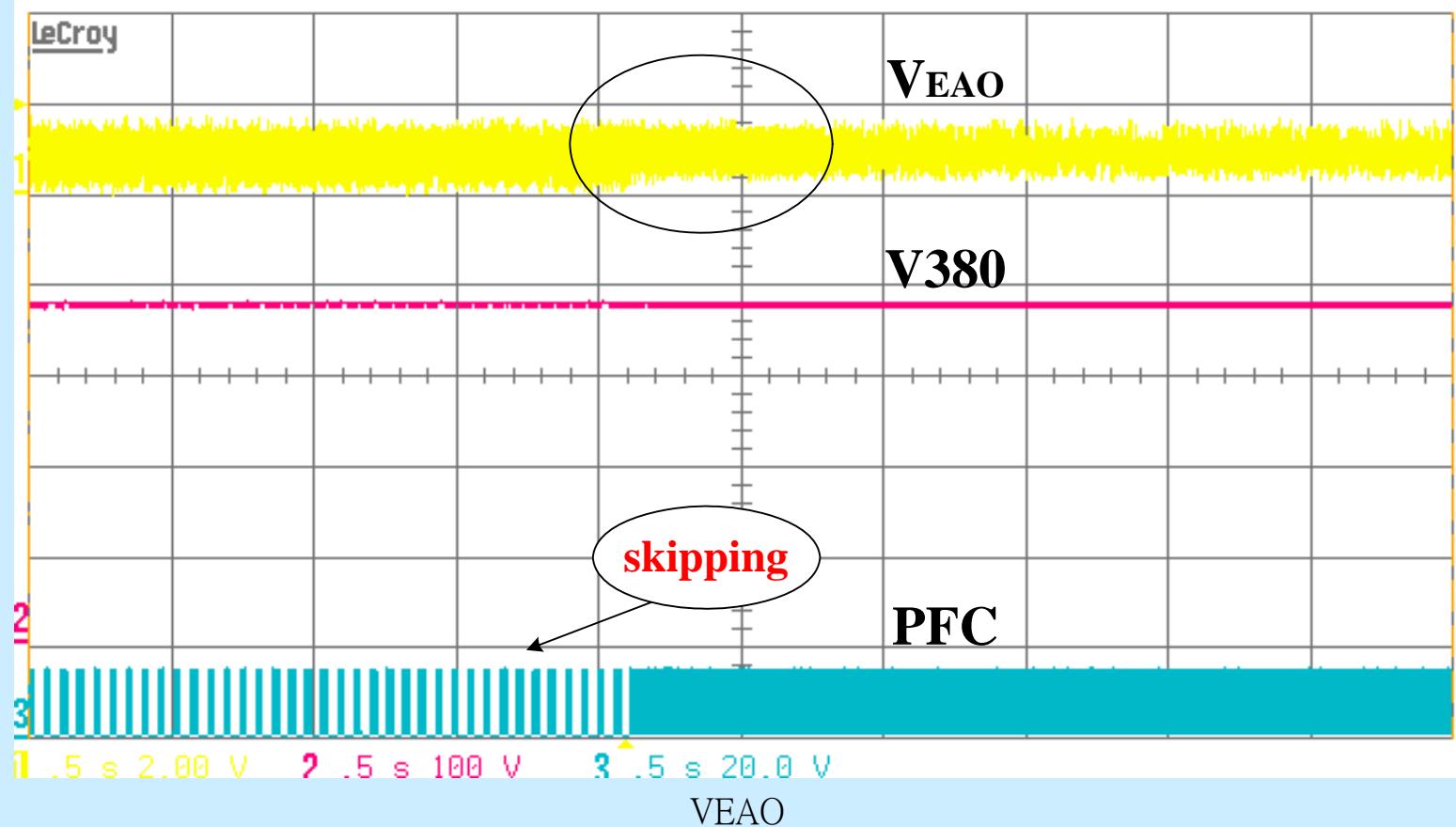


If  $V_{EAO} < 0.3$  PFC pulse skipping

# PWM turn-on-off

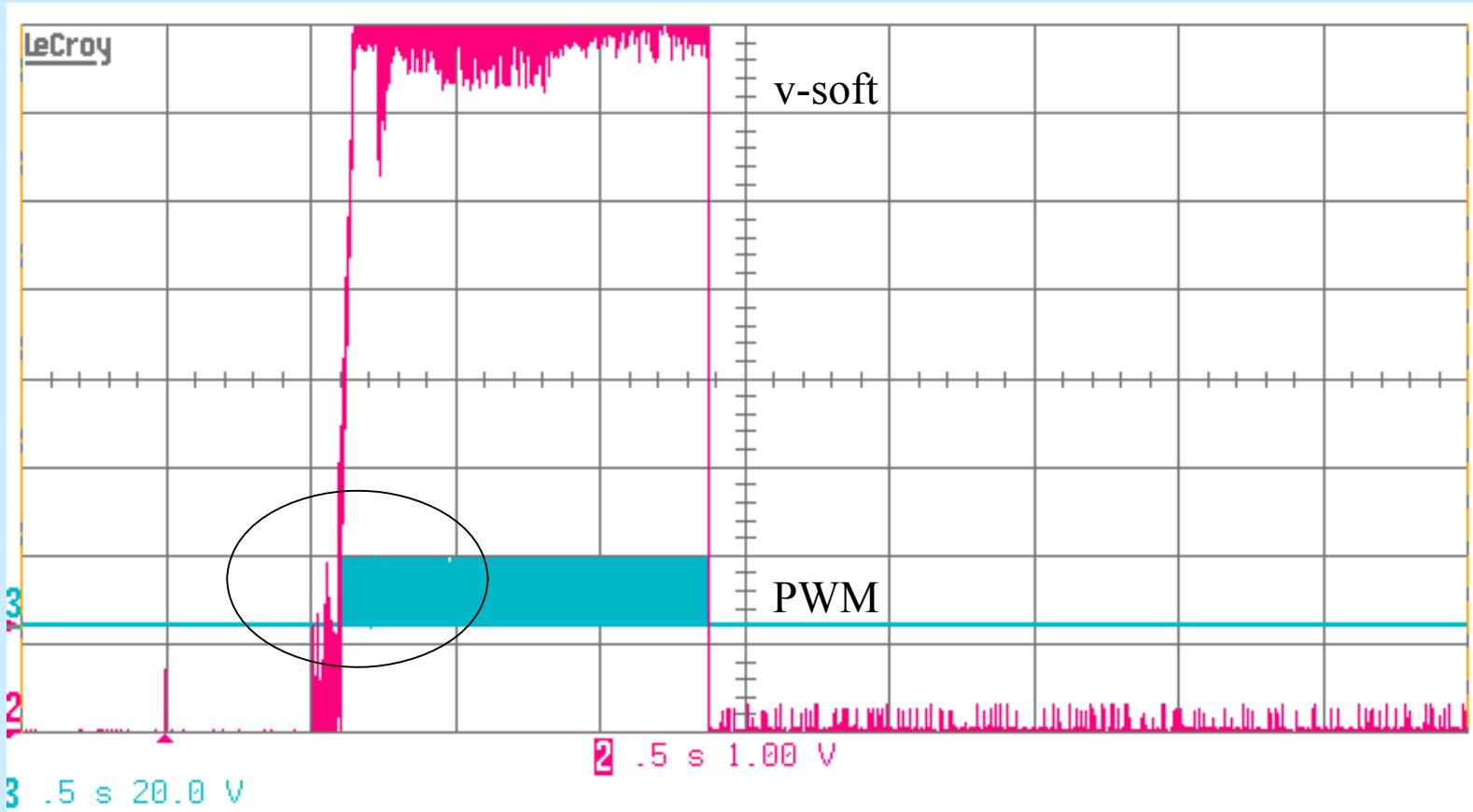


- $V_{soft} > 1.25V \rightarrow$  PWM turn-on
- $V_{soft} < 1.25V \rightarrow$  PWM turn-off

# PFC-PWM timing

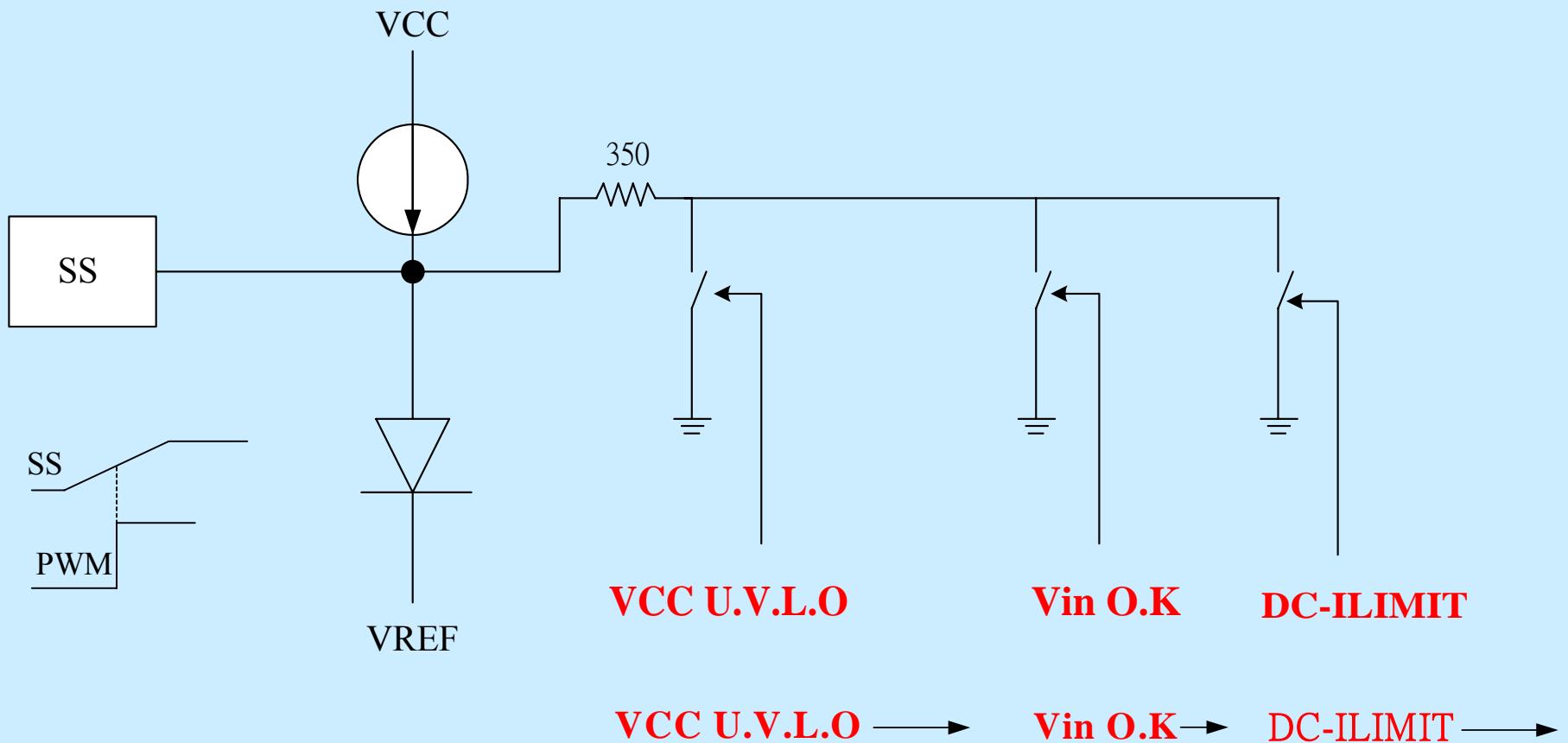


# PFC-PWM timing waveform

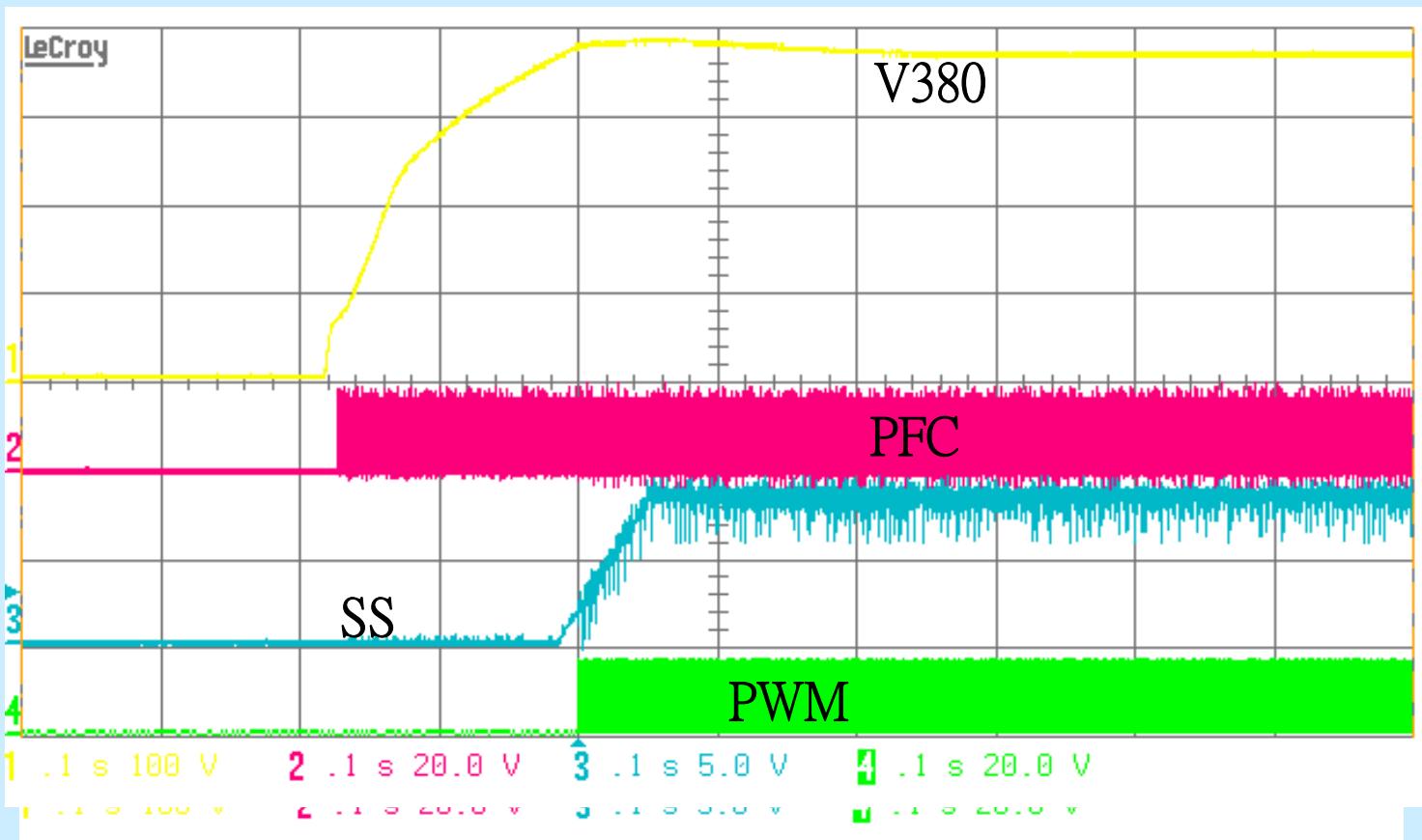


# VCC O.V.P


O.V.P

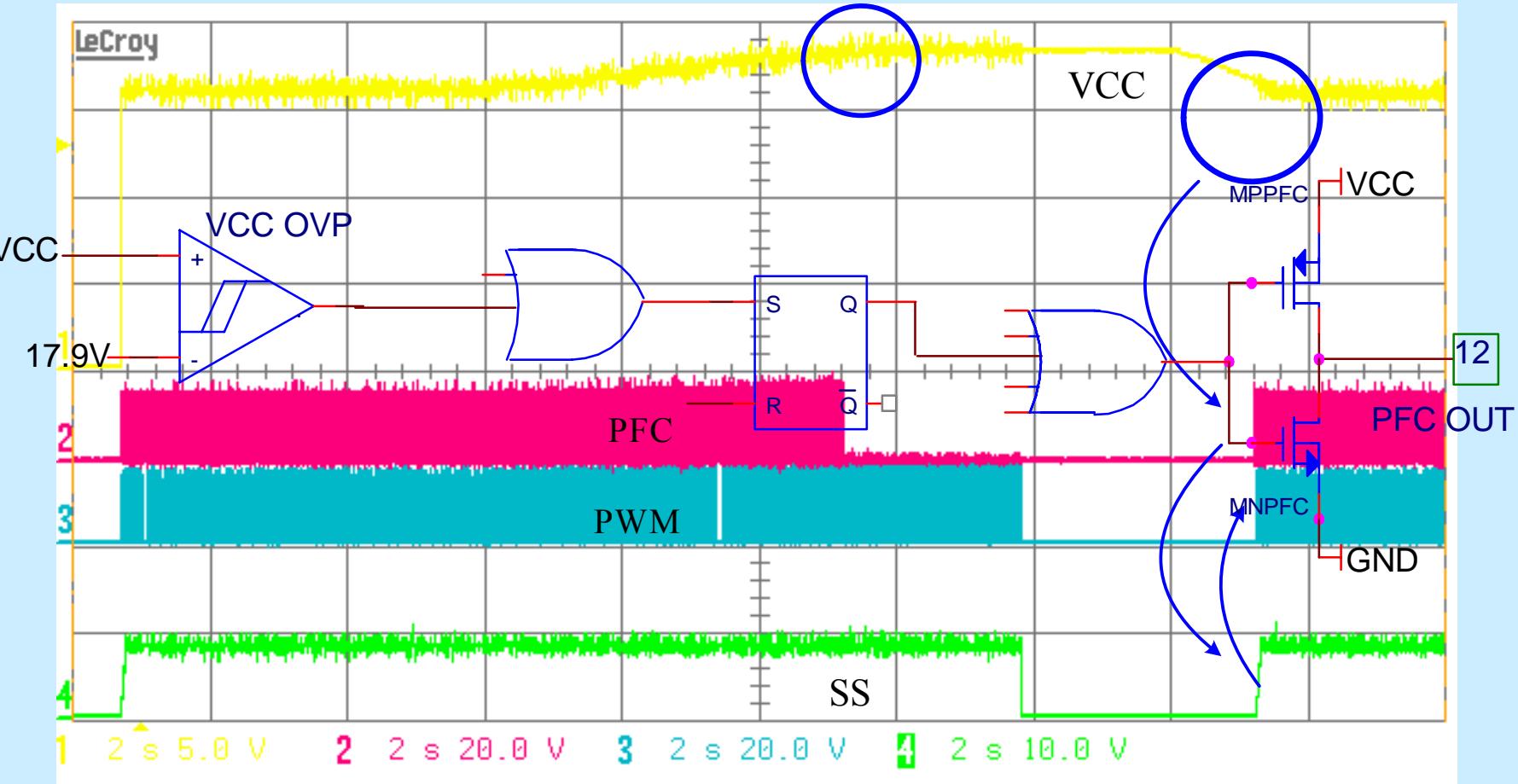

# VCC U.V.L.O

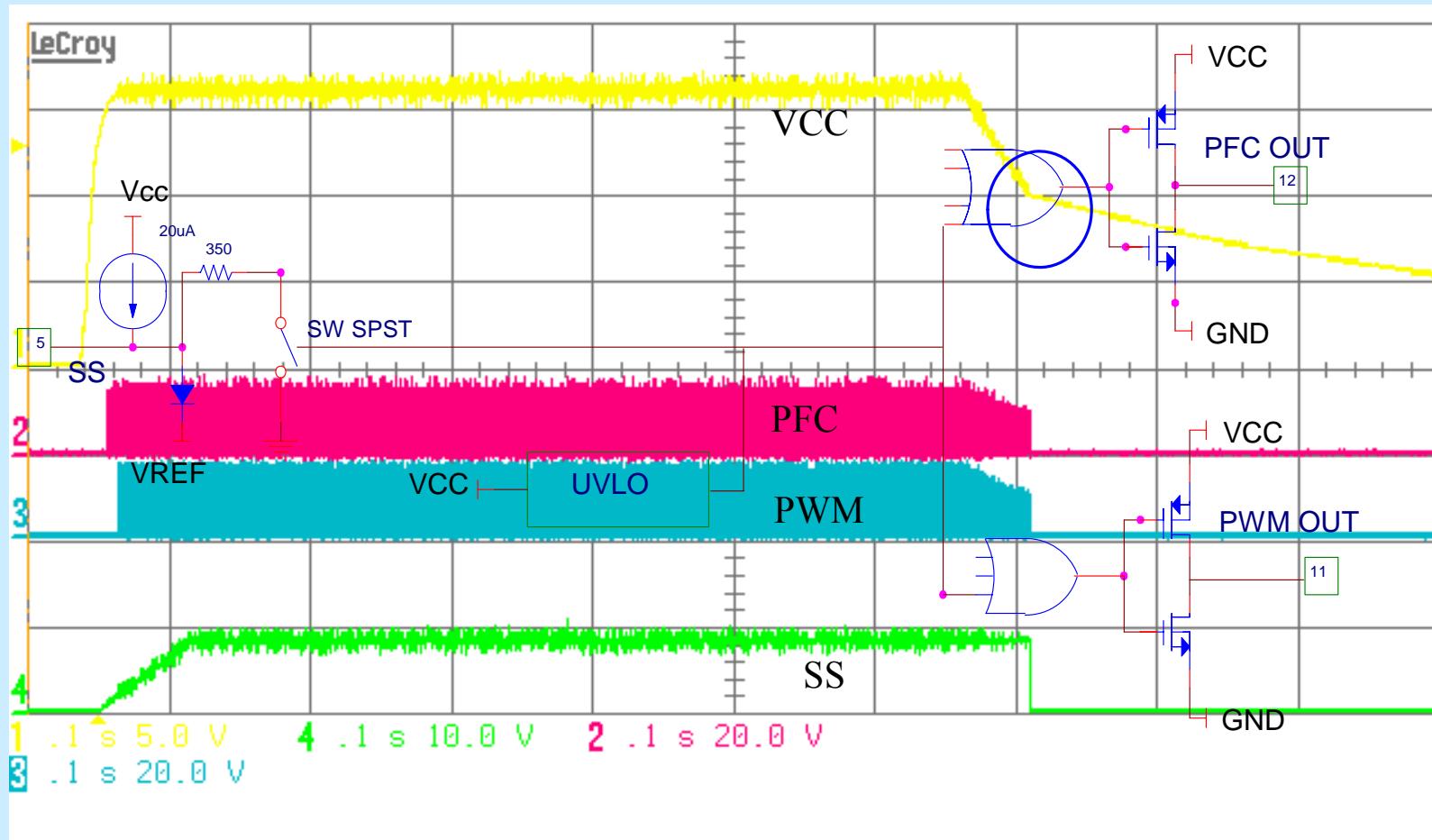


# PWM current limit

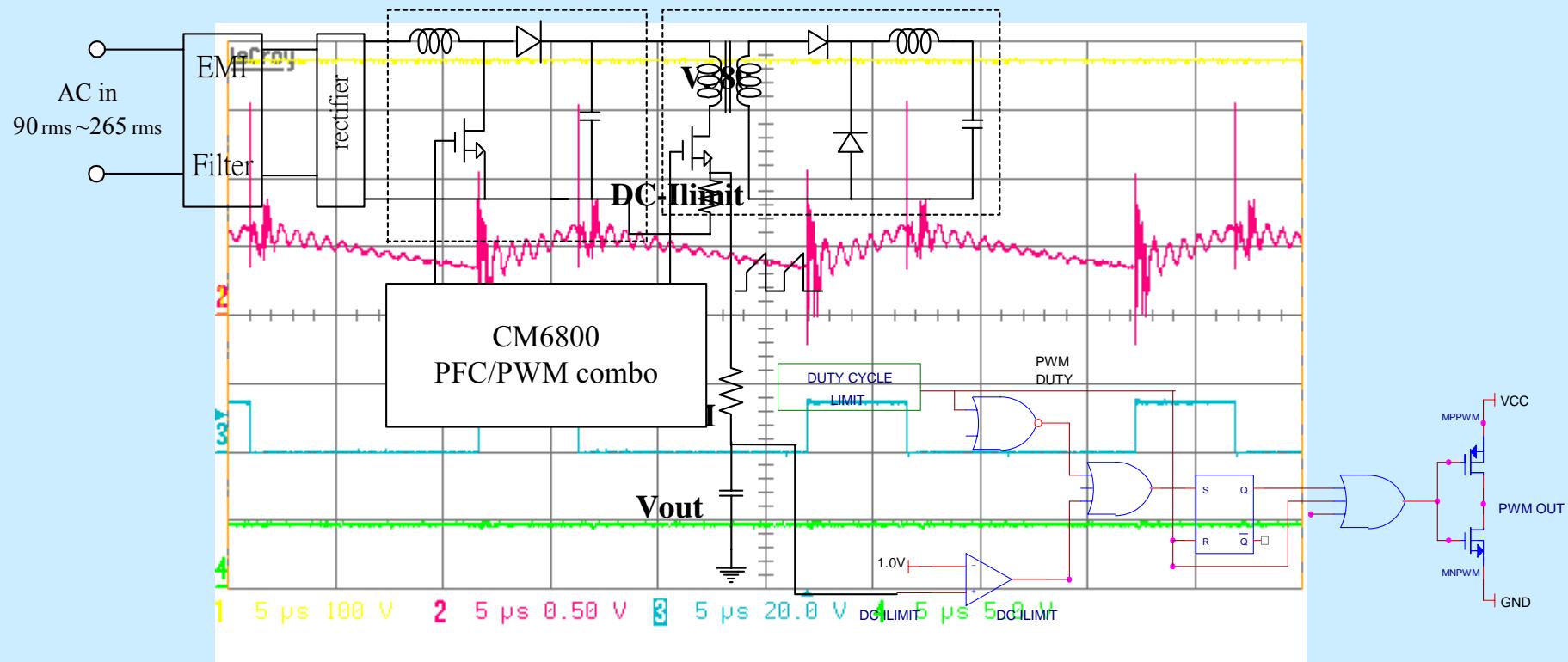



PWM duty cycle by cycle reduce

# DC-Ilimit current waveform

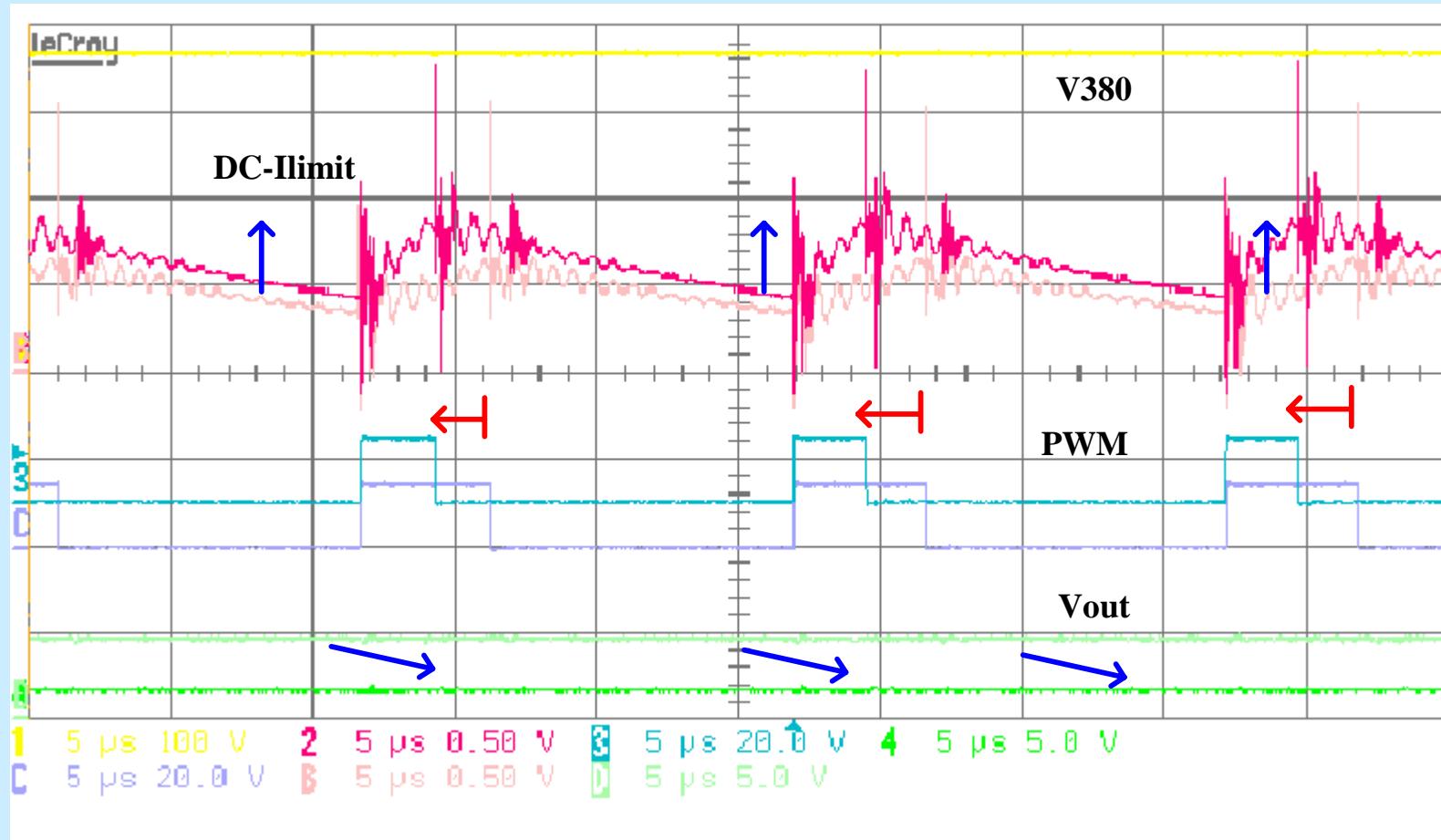



# Waveform discuss

PFC(leading-edge)

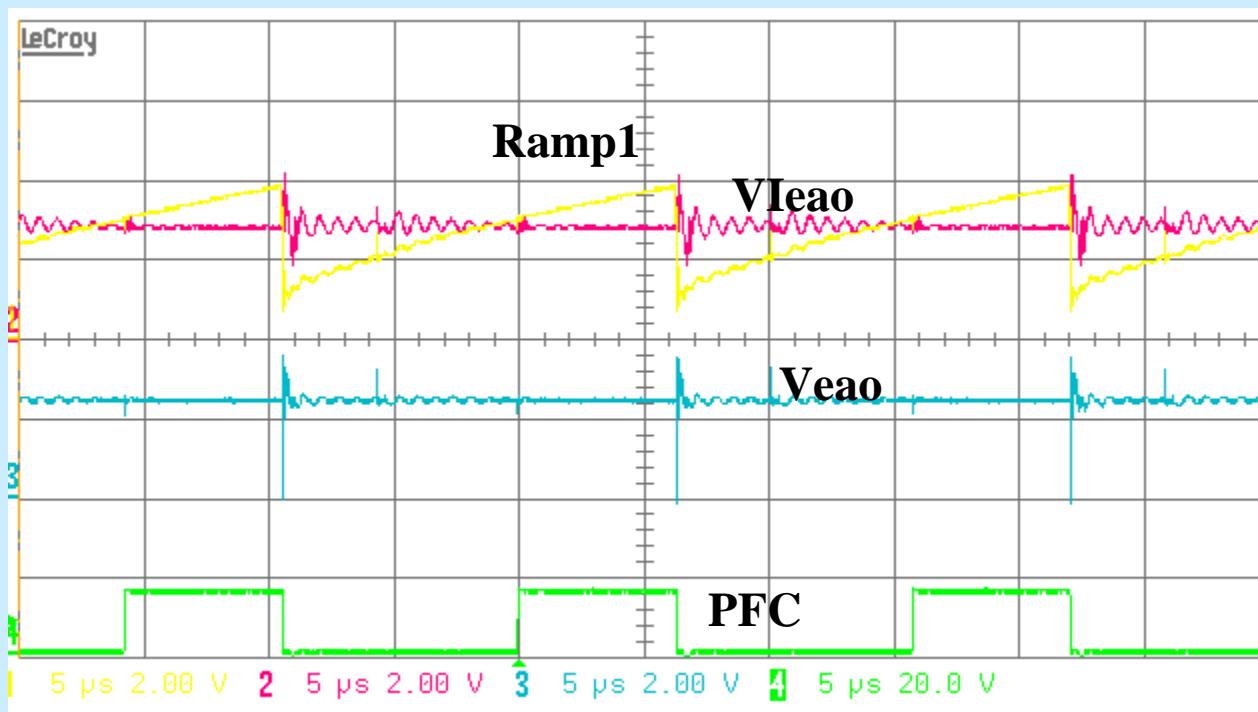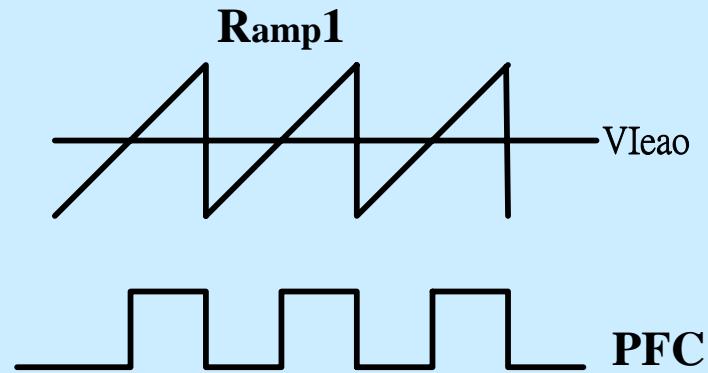

# Waveform discuss

PWM(trailing-edge)

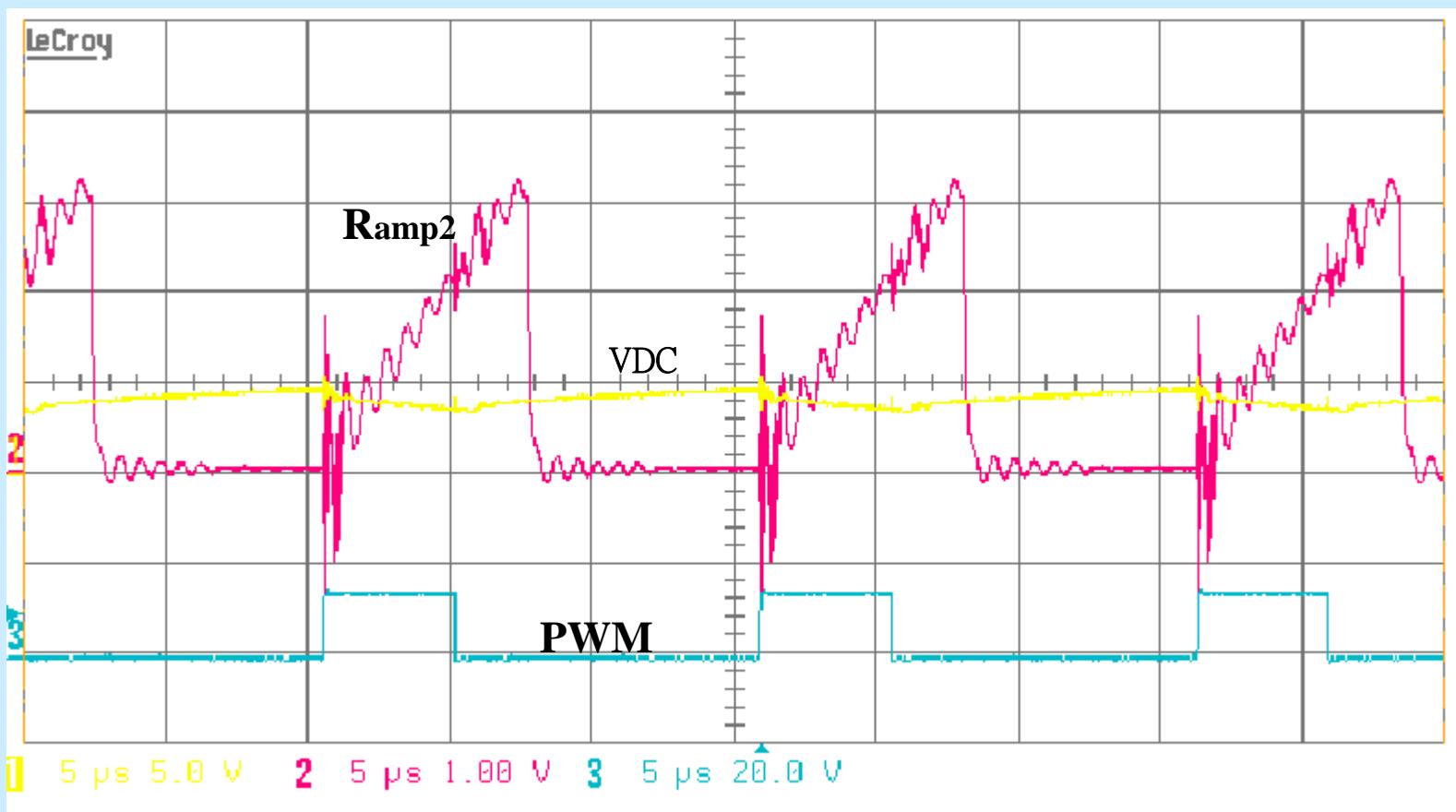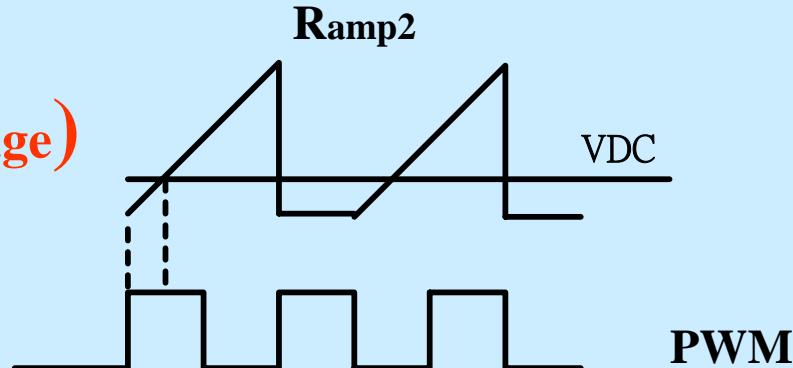


# Disable CM6800


**PFC:Veao pull-low**

**PWM:Soft-start pull-low**


# Summary

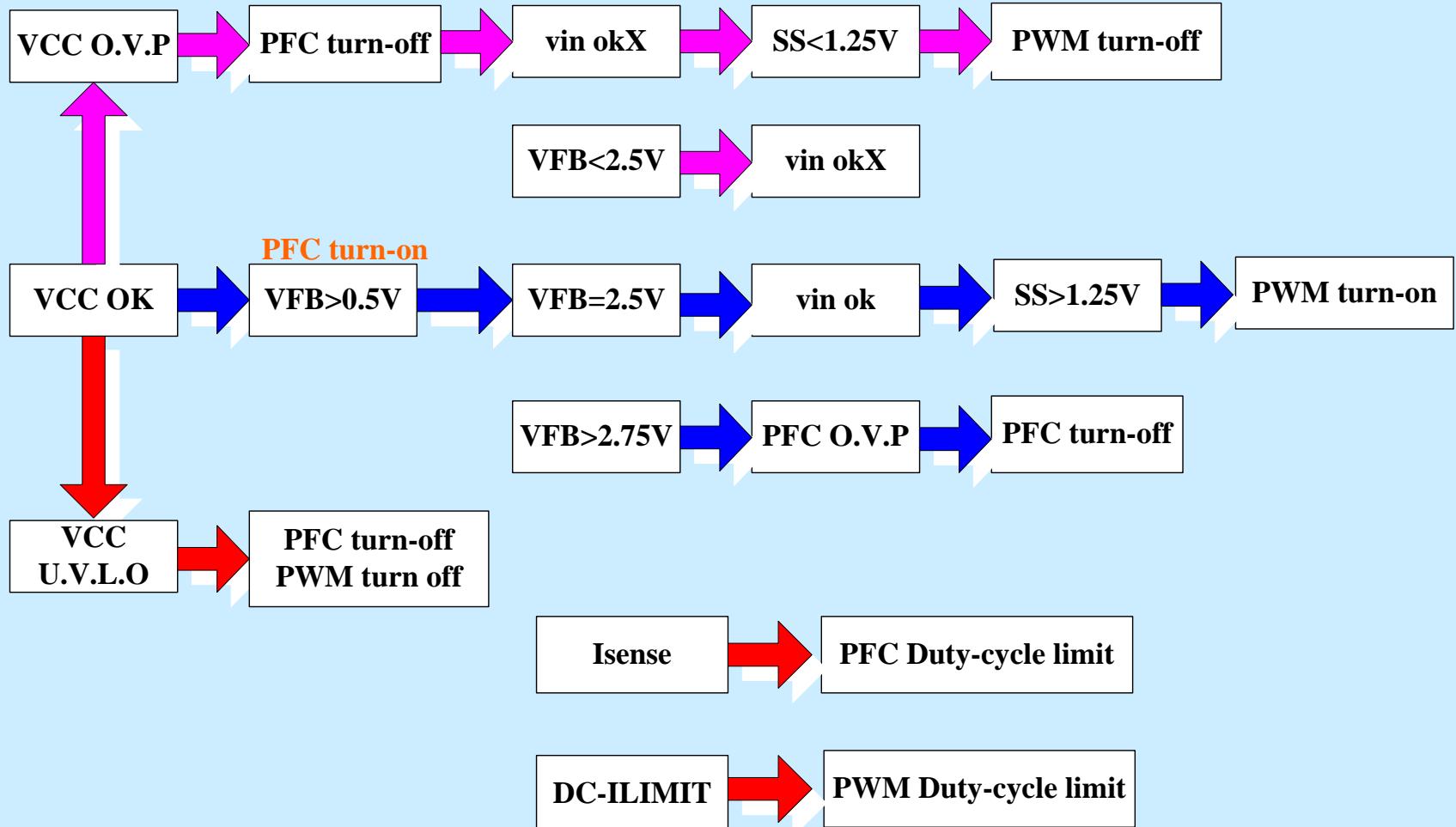

## Control 1

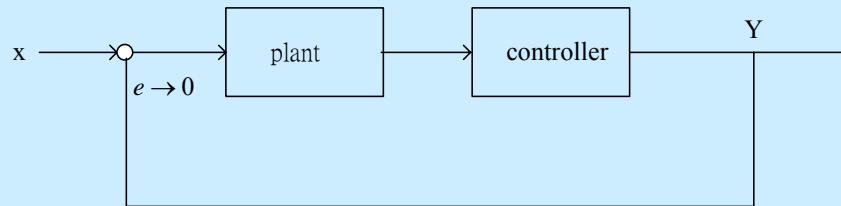


## Control 2

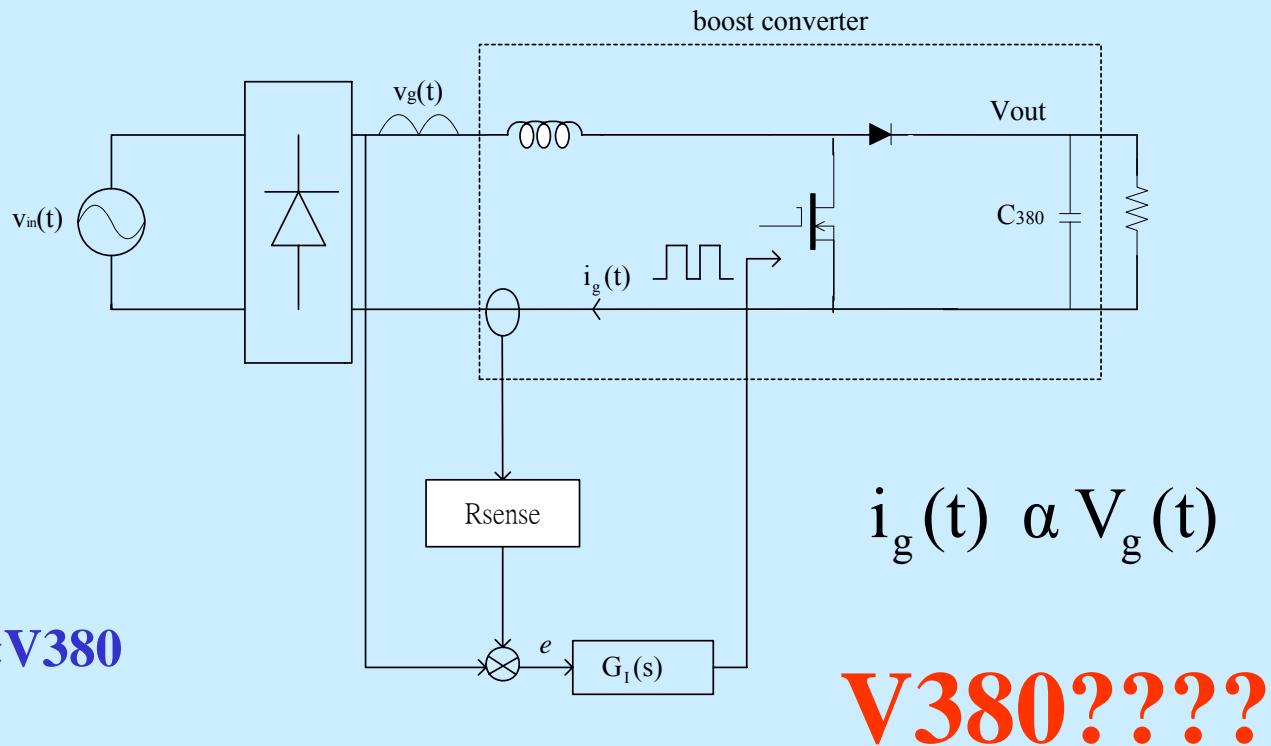


Goal:P.F&V380

V380????

# PFC&regulation

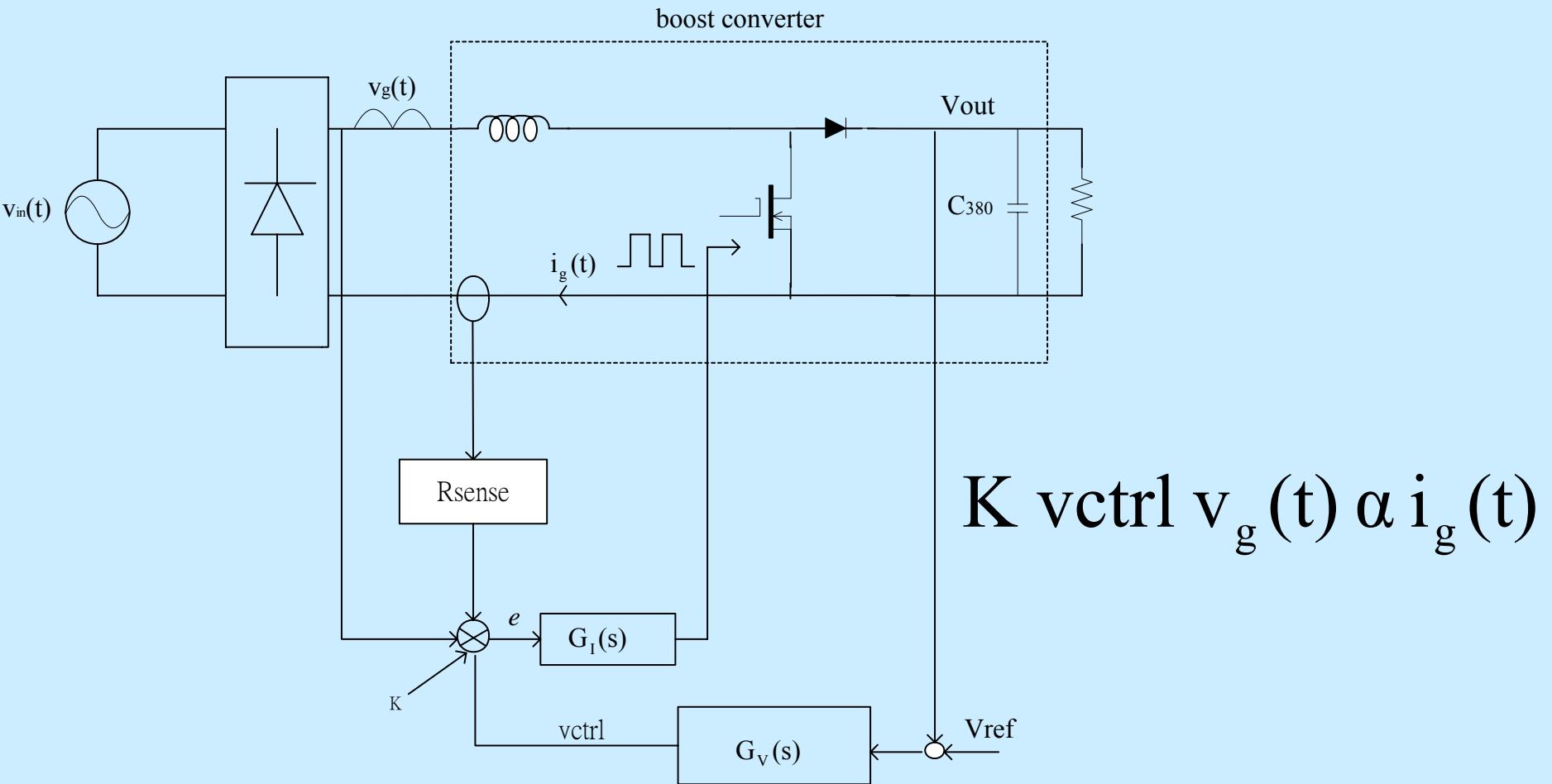


# PFC&regulation

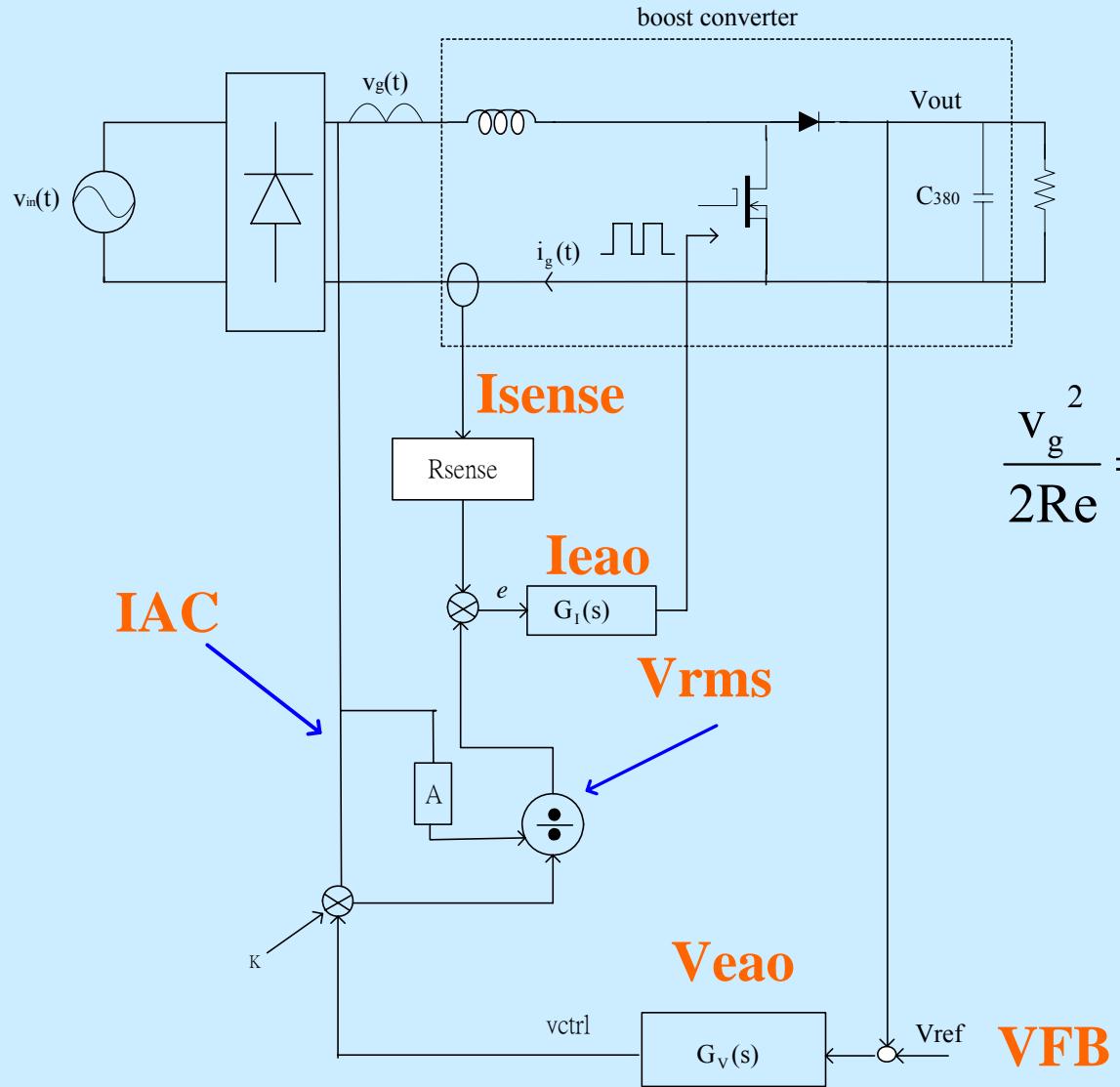

$$\frac{V_g^2}{2R_{\text{Re}}} = \frac{V_{380}^2}{R_L} \xrightarrow{A} \frac{V_g^2}{2A R_{\text{Re}}} = \frac{V_{380}^2}{R_L}$$

$$A = V_g^2$$

# 6800 circuit

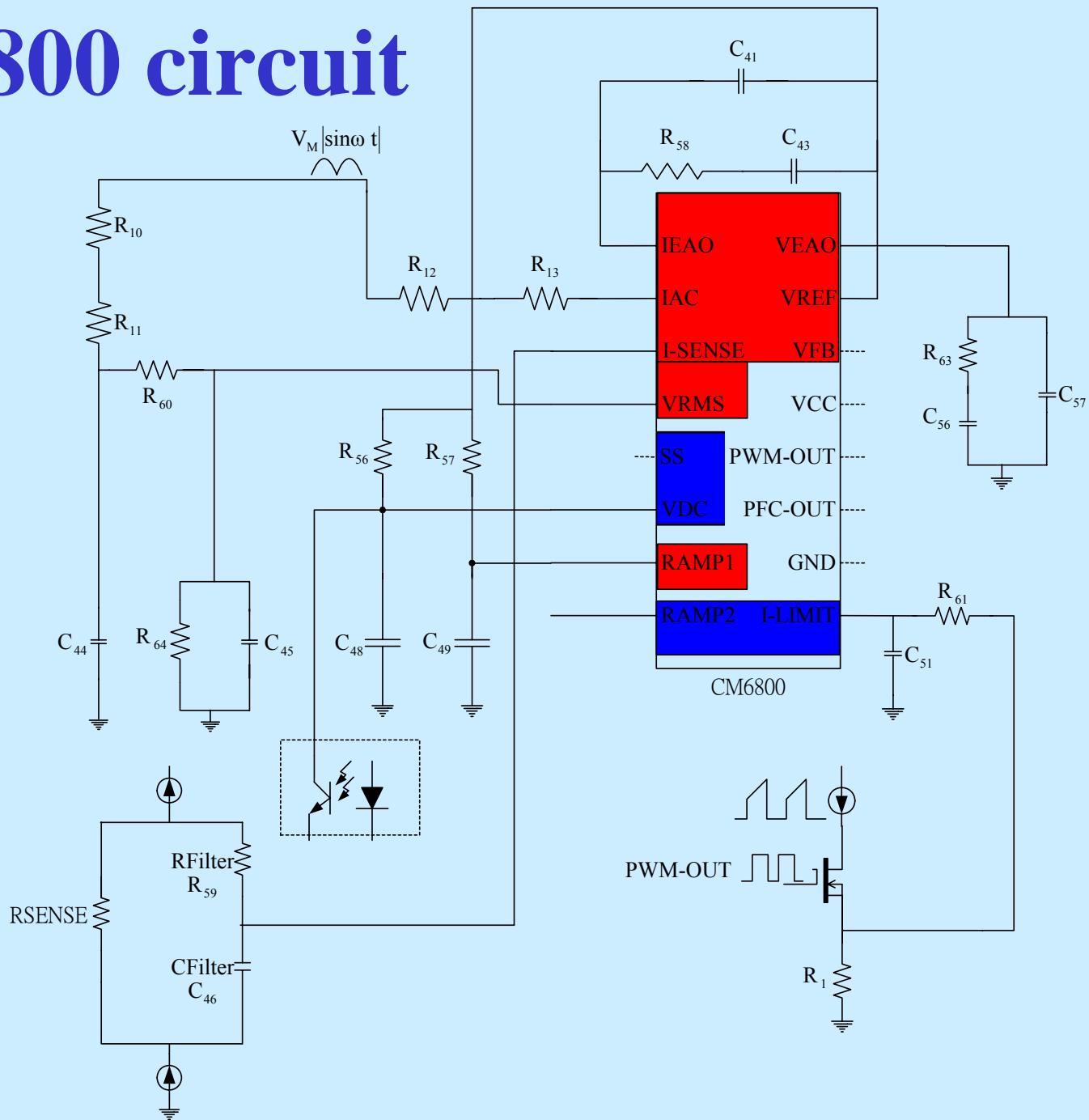

The diagram consists of two rectangular blocks. The top block is red and labeled "PFC". The bottom block is blue and labeled "PWM".

# Note

**Note:AC to DC**


**Compensation rule**

**Reference CM6800 compensation word files**

INPUT POWER	W		74.746	
PF	%		0.869	
INPUT AC VOLTAGE	V		230.66	
INPUT CURRENT	A		0.373	
FREQUENCY	Hz		50.061	
+5V LOADING	A			
+12V LOADING	A			
-5V LOADING	A			
-12V LOADING	A			
+3.3V LOADING	A			
+5Vaux LOADING	A			
Po			0	
EFFIENCY			0%	
N	A	READING	SPEC.	%
3	0.254136	0.07146	0.25	28.20%
5	0.142017	0.01806	0.14	12.75%
7	0.074746	0.01351	0.07	18.13%
9	0.037373	0.01069	0.04	28.69%
11	0.026161	0.00575	0.03	22.04%
13	0.022136	0.00727	0.02	32.94%
15	0.019185	0.00896	0.02	46.84%
17	0.016928	0.00152	0.02	9.01%
19	0.015146	0.00656	0.02	43.44%
21	0.013703	0.00474	0.01	34.69%
23	0.012512	0.00115	0.01	9.22%
25	0.011511	0.00397	0.01	34.59%
27	0.010658	0.00394	0.01	37.07%
29	0.009923	0.00172	0.01	17.38%
31	0.009283	0.0017	0.01	18.37%
33	0.00872	0.0034	0.01	39.10%
35	0.008222	0.00226	0.01	27.57%
37	0.007778	0.00105	0.01	13.54%
39	0.007379	0.00326	0.01	44.31%


# Harmonic

Harmonic

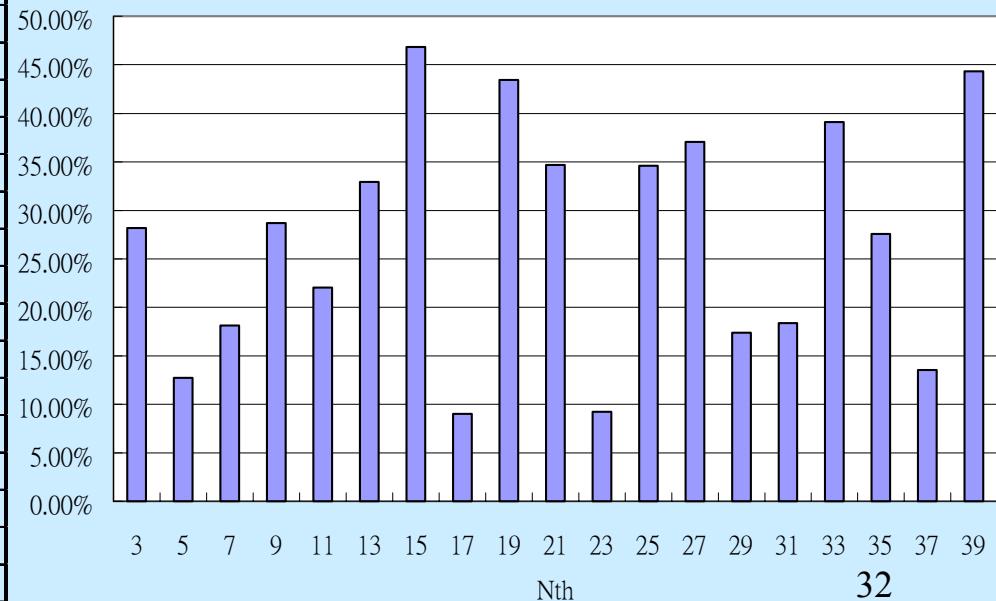


# Power factor

90VAC @ Max3.16A

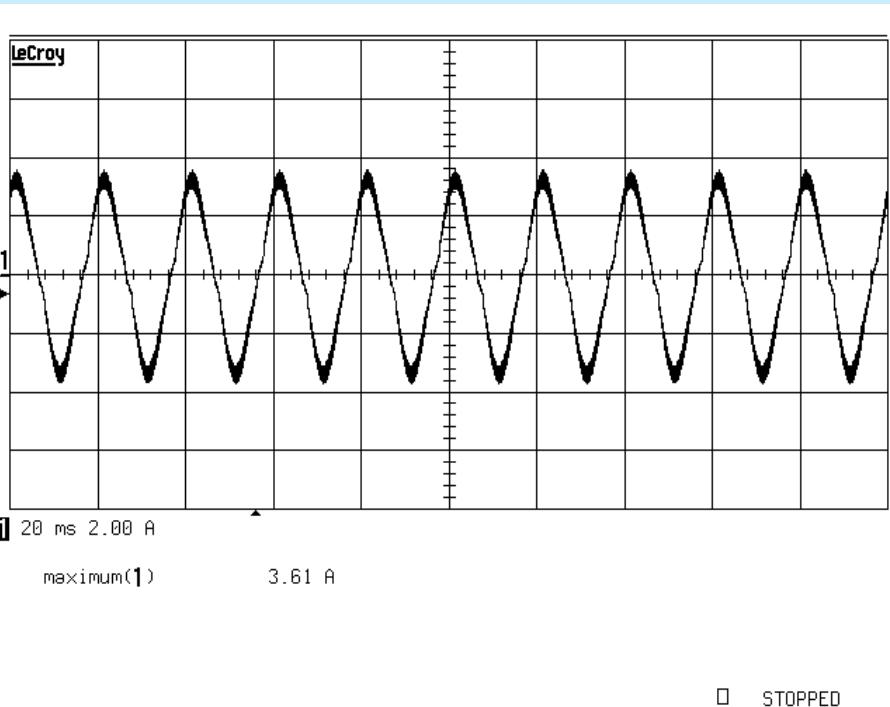

264VAC @ Max3.16A

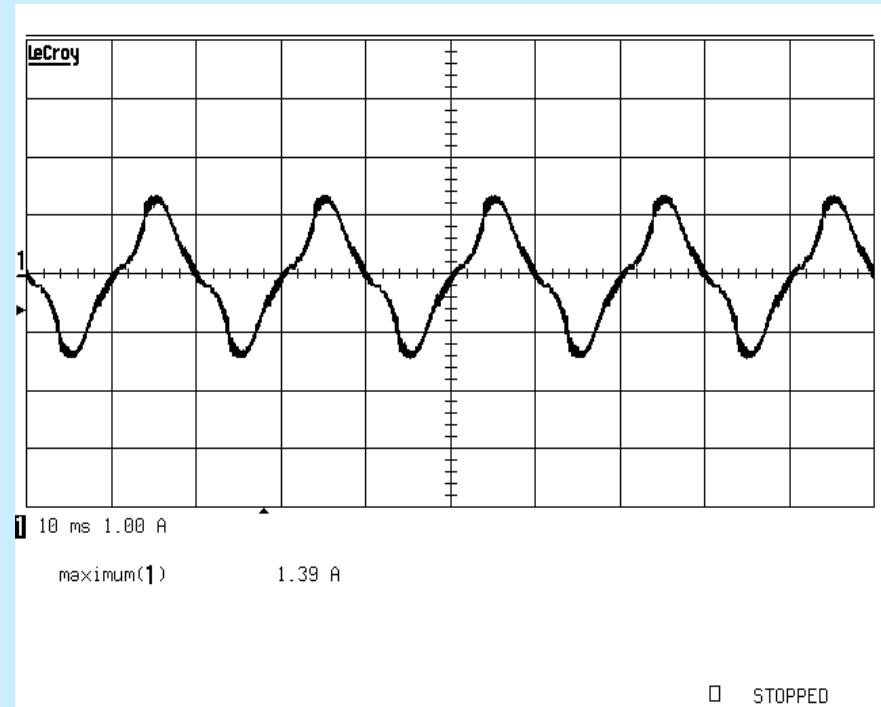

# Summary

