

**Define Market**

- Low Cost PC Power/Clone PC market
- Replace Passive PFC with Active PFC
- Single Range (230Vac only) Power (70% market share)

**Topology+controller**

**Passive to Active PFC using CM6805A/B**


- PFC + Single Switch Forward, Dual Switch Forward (base on purchase capability)
- fixed switching frequency (67.5Khz or 100Khz)
  - CM6805A/B: 10 pin SOIC fpfc = fpwm = 67.5Khz(05A) or 100Khz(05B)

## Why chose 6805 series replace passive power supply(cost???)

### CM6805 family could drive BOM 20% lower than 6800A


- \$ 10 pin SOIC PFC/PWM combo allows Less external components (about 14 components less)
- \$ Leading Edge PFC/Trailing Edge PWM → 450V Bulk Cap can be reduced
- \$ Digitized PWM maximum duty, 50% → 450V Bulk Cap can be further reduced
- \$ CM6805 specialized feature with Powder Iron PFC core(230V AC)
- \$ Single Range Power reduces PFC Mosfet
- \$ Passive PFC has the higher cost in shipping
- PFC tri-fault and PWM tri-fault →UL1950 (Passive PFC cannot meet it)
- No load consumption spec. cannot be met by Passive PFC; Easy for CM6805 family
- Smooth On/Off which single PFC with single PWM is difficult
- \$ As results, the BOM cost is lower than Passive PFC

Feature how to reduce power cost

 


A Cascade Boost-Buck Power Converter Without Synchronous Switching

 
Leading Edge Modulation PFC and Trailing Edge Modulation PWM for PFC Output Ripple Reduction



 Synchronous Switching Cascade Power Converter



Boost Stage with a Constant Current Loss

 


Cascade Power Stage with Synchronous Switching

•Bulk Cap. up to savings \$:0.2




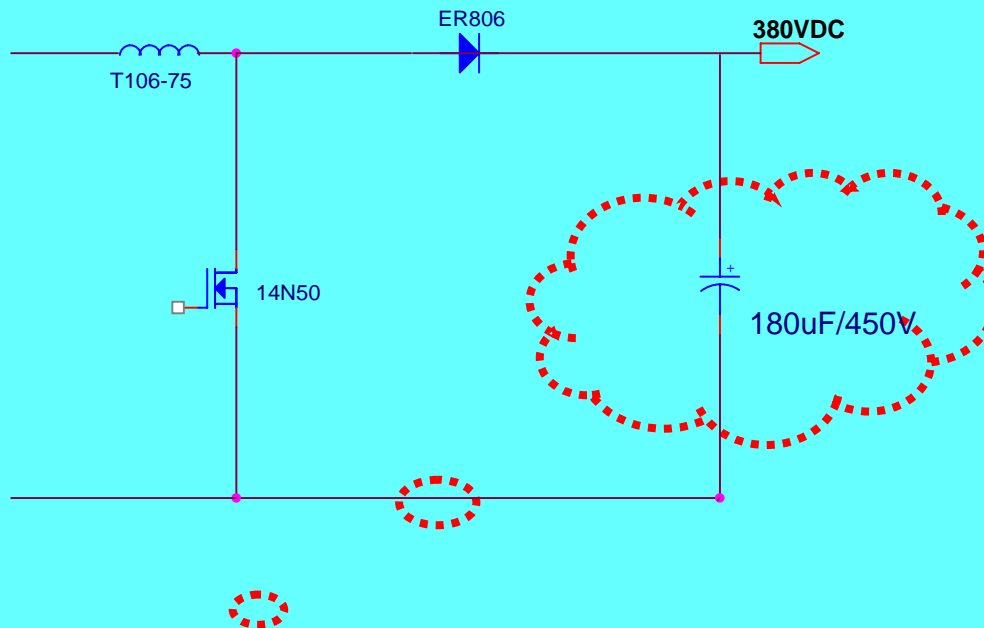
**Digitized PWM maximum duty, 50%**  
**→450V Bulk Cap can be further reduced**



V tolerance  $\pm 20\%$  ~ tolerance (0)

M tolerance  $-10\%$  ~  $+20\%$  (x)

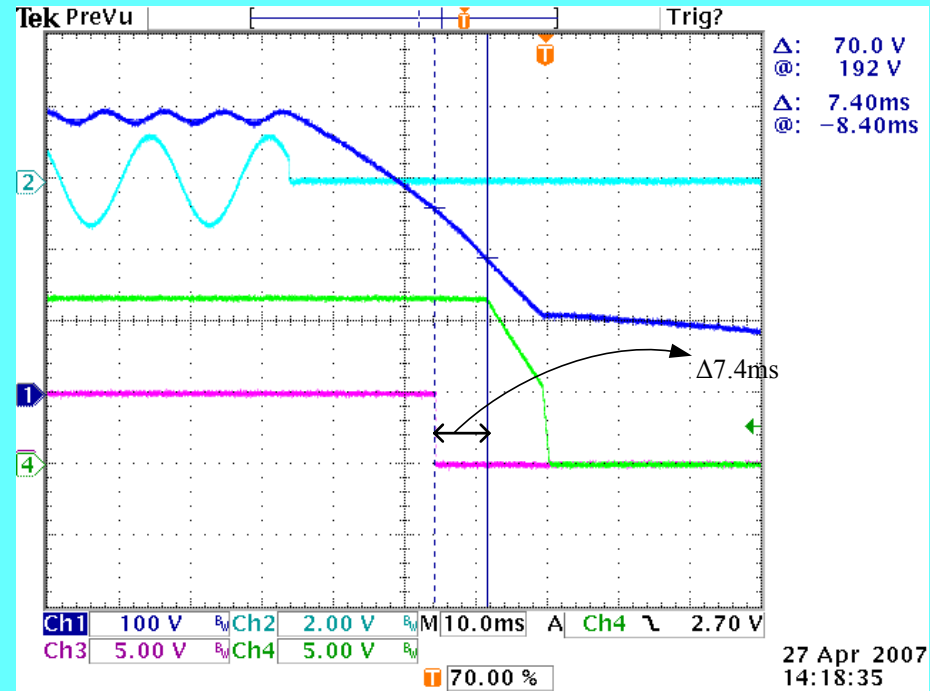 
V tolerance (V) Bulk cap up to \$:0.05(7%) savings




**Hold up time can gain 6ms least, still keep PG to main output >1ms lead(1.4ms).**



### Control 1

 



### Control 2

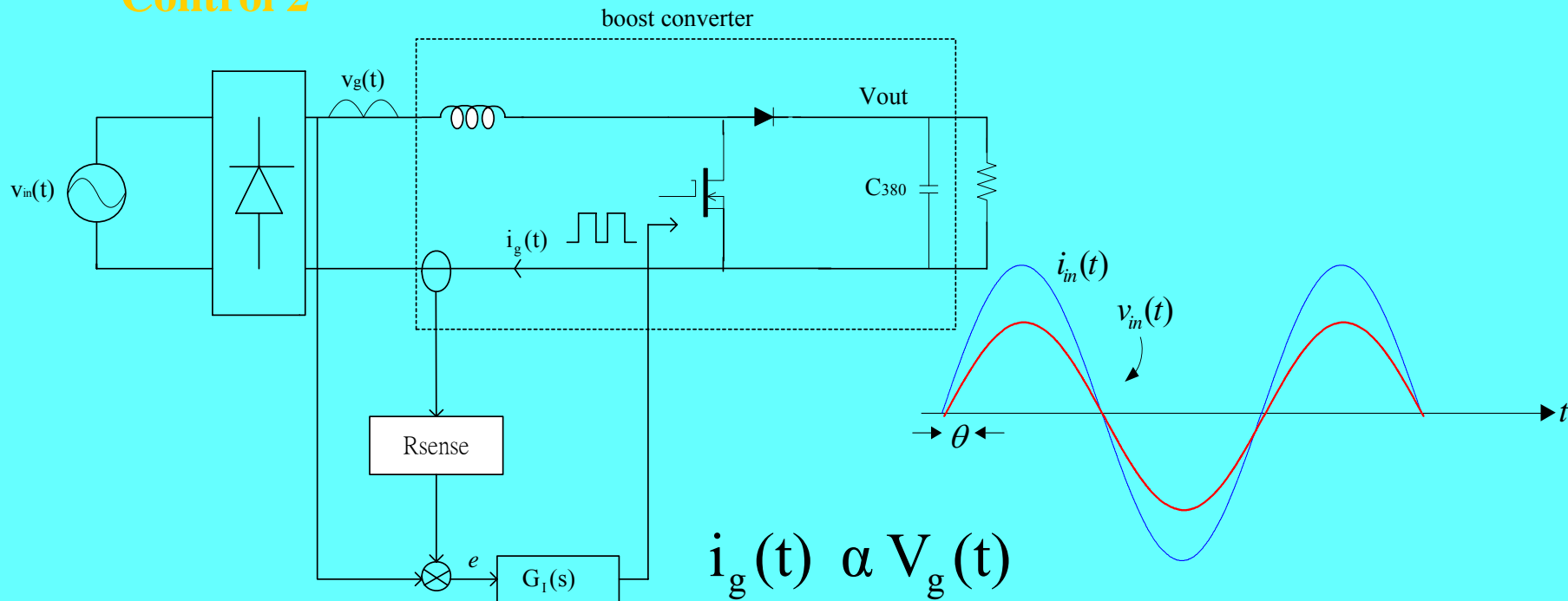

# V380????



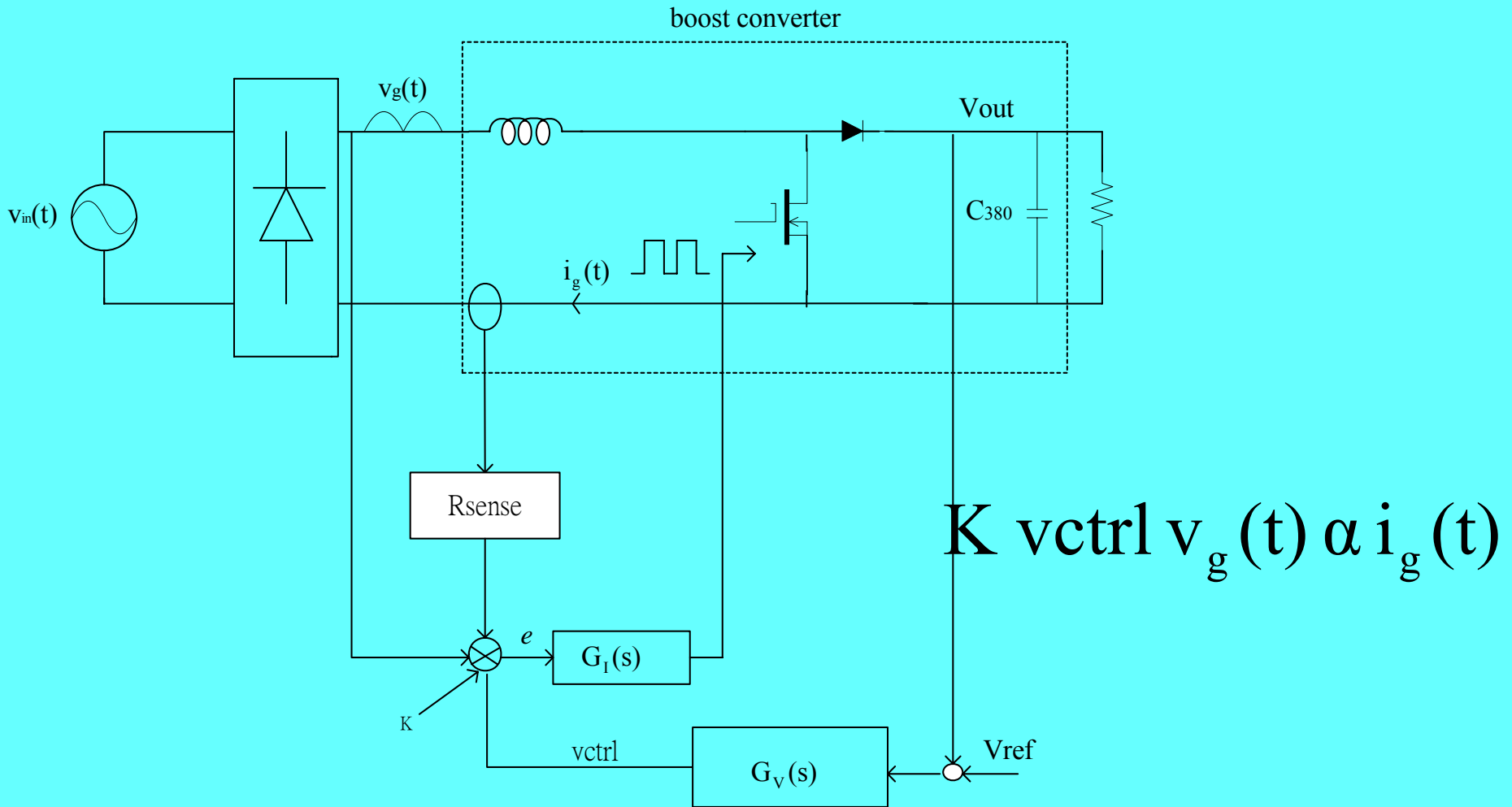

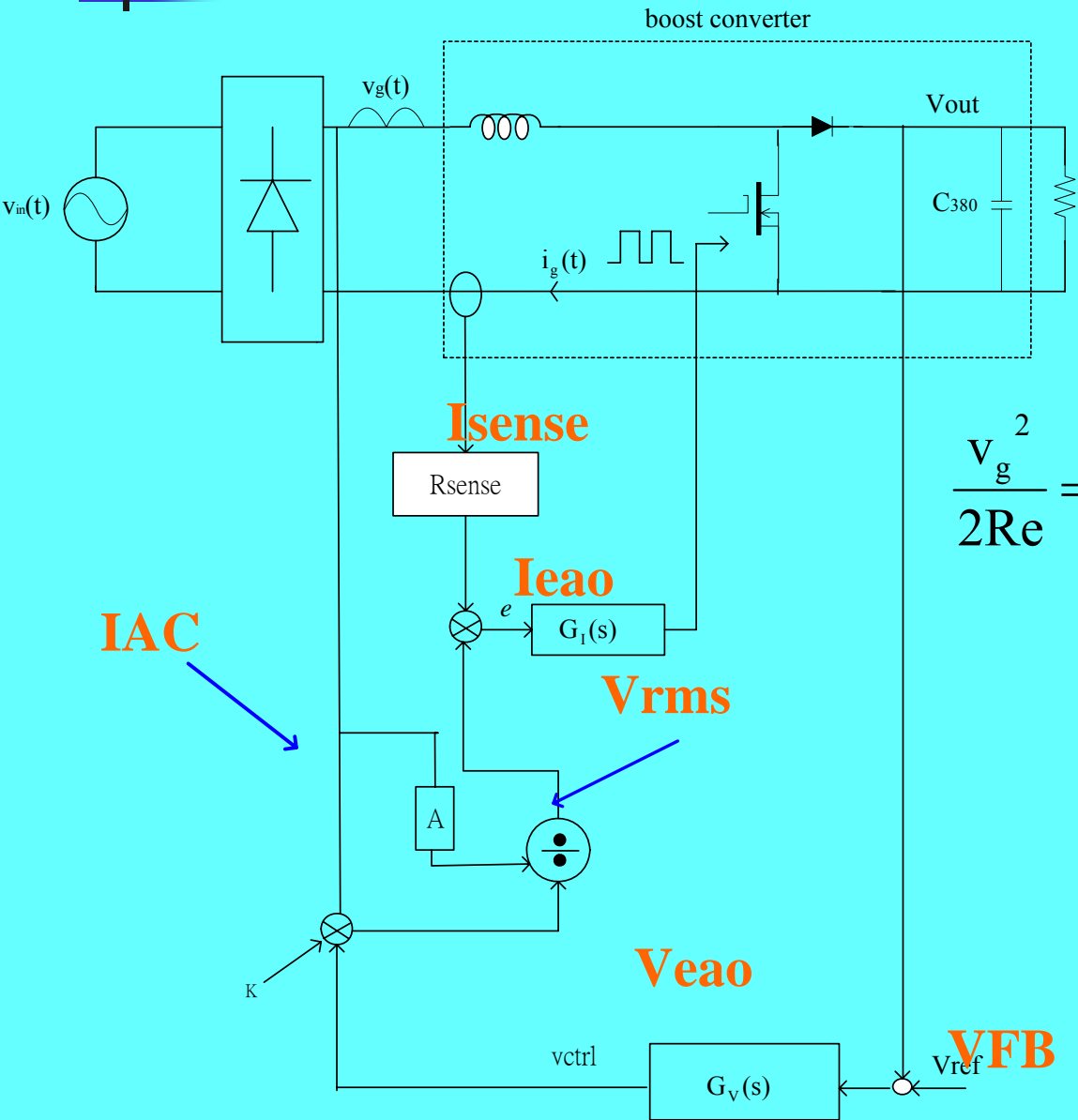

$$\frac{v_g^2}{2Re} = \frac{V_{380}^2}{R_L} \xrightarrow{A} \frac{v_g^2}{2ARe} = \frac{V_{380}^2}{R_L}$$

$$A = v_g^2$$

**IAC**

**Isense**



**Iea0**

**Vrms**



**Veao**

**VFB**

## PFC(Leading-edge)

  





## PWM(trailing-edge)

 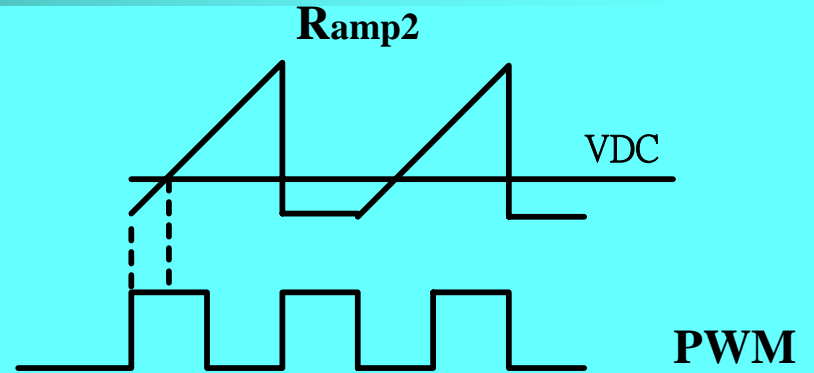


# **CM6805A/B/CM6903 PFC Controller:**

**Leading Edge Modulation  
with Input Current  
Shaping Technique**

**(I.C.S.T)**

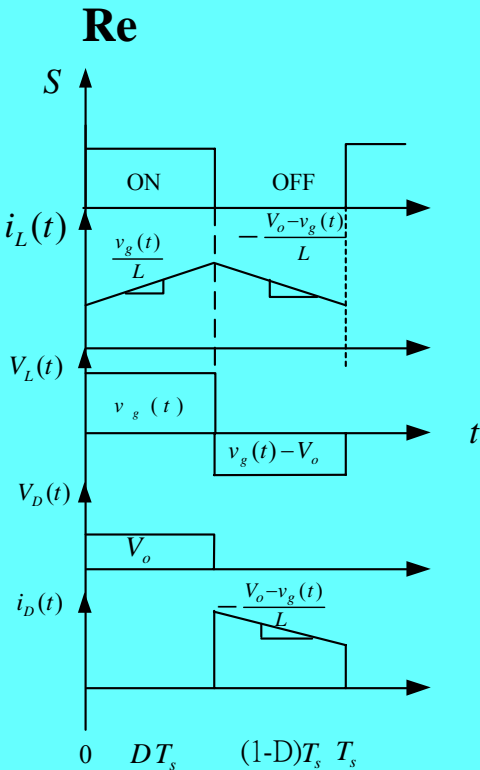   

$$R_e = \frac{V_g}{i_g}$$

 

$$\langle i_g \rangle = \langle i_L \rangle$$


$$v_g \times \langle i_L \rangle \approx V_{out} \times \langle i_d \rangle$$

$$\langle i_d \rangle = \frac{(1-d)^2 \times V_{out}}{R_e}$$

$$\frac{V_{out}}{V_g} = \frac{1}{(1-d)}$$

$$\langle i_d \rangle = \frac{V_{out}}{R_e} \times \frac{t_{off}}{T_{sw}}$$

# Championmicro

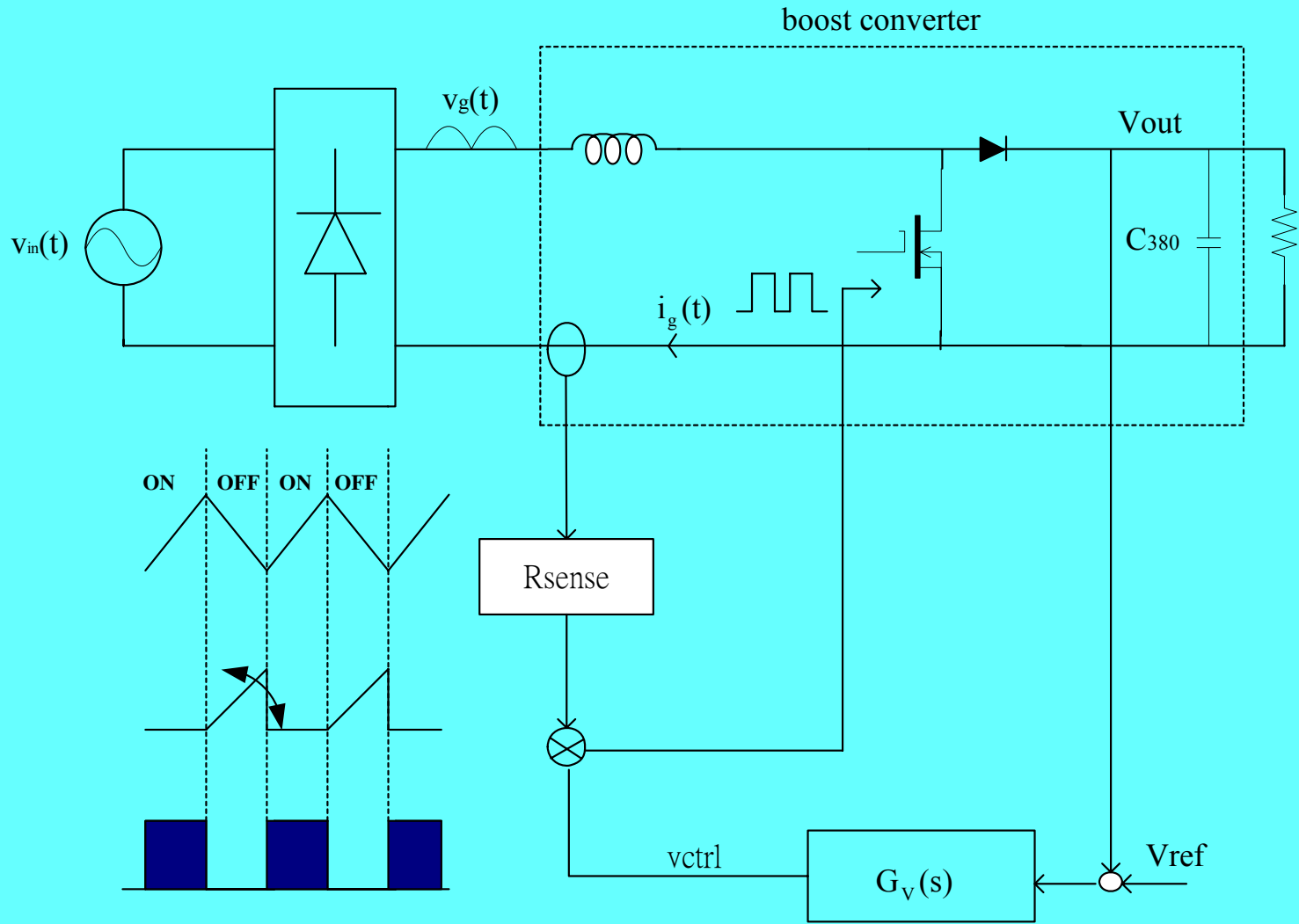





- Rac 作為slope compensation斜率補償用
- 調整作為THD enhance
- Rac以IC內部阻值作為選擇依據

Iac impedance	Rac	Part.No.
40k	4~6M	CM6805A

- Isense 之訊號需filter 為 1/6~1/10 switching frequency


$$Isense_{frequency} = \frac{1}{2\pi \times R_{is} \times C_{is}} = \frac{1}{6} \sim \frac{1}{10} f_s$$

$R_{is}$  選用47Ω


$$= \frac{1}{2\pi \times 47 \times C_{is}} = \frac{1}{6} \sim \frac{1}{10} f_s = 6750$$

$$C_{is} = 301.1n \sim 50.9nF$$


可選用0.1μF

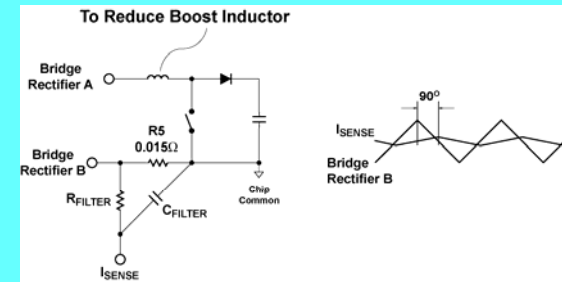

## PFC Soft Star

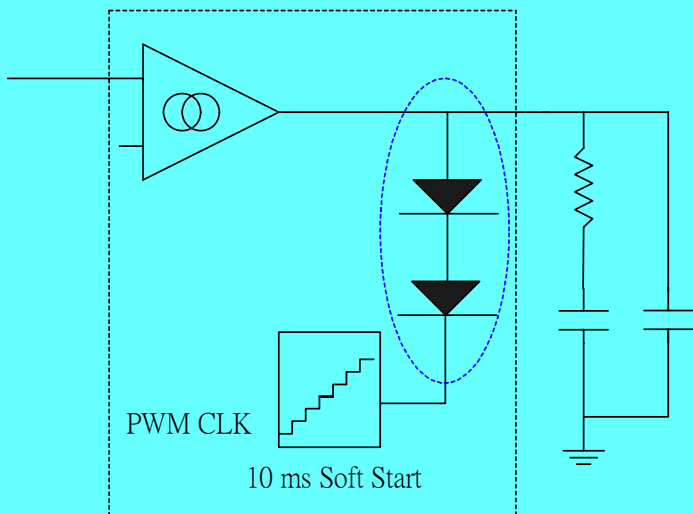


**CM6805A/B**

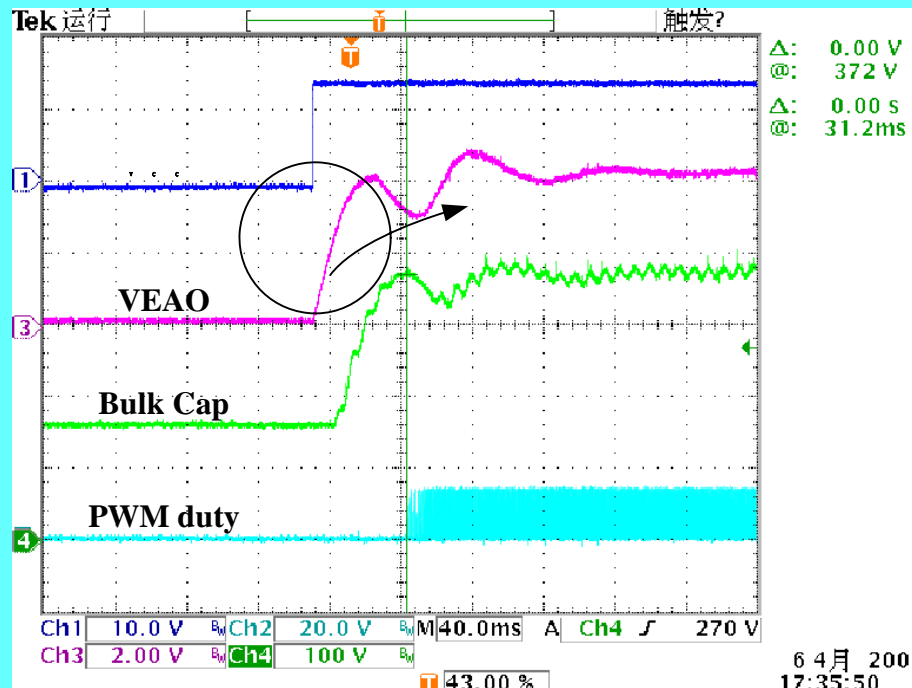

6 4月 2007  
17:35:50

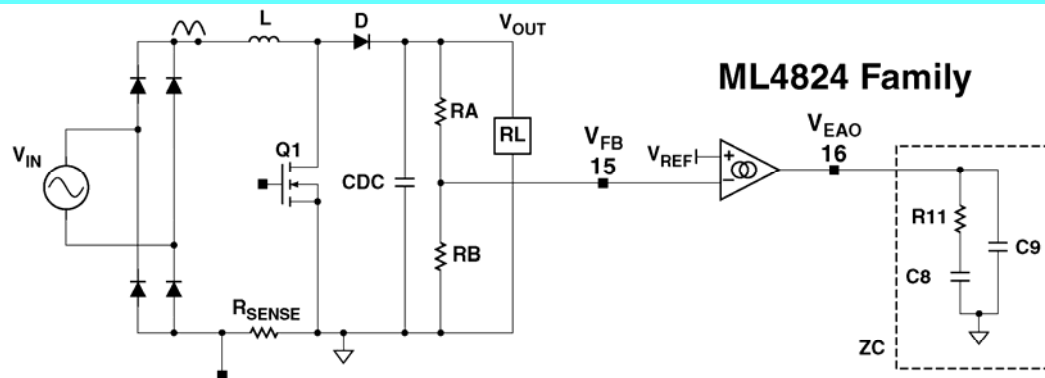- VEAO的補償為乘上zero-pole network，一般選擇其unity-gain(crossover-frequency)為0.5 line-frequency=25Hz or 30Hz，zero的位置為0.1pole。



$$\therefore \frac{\Delta V_{OUT}}{\Delta V_{EAO}} = \frac{P_{IN \text{ AVERAGE}}}{V_{OUT} \times \Delta V_{EAO} \times S \times C_{DC}} \quad (1)$$

$$\therefore \frac{\Delta V_{FB}}{\Delta V_{OUT}} = \frac{R_B}{R_A + R_B} = \frac{2.5V}{380V} \quad (2)$$

$$\therefore \frac{\Delta V_{EAO}}{\Delta V_{FB}} = G_m \times Z_C \quad (3)$$


$$\therefore \text{Loop Gain} = \frac{\Delta V_{OUT}}{\Delta V_{EAO}} \times \frac{\Delta V_{FB}}{\Delta V_{OUT}} \times \frac{\Delta V_{EAO}}{\Delta V_{FB}} = \frac{P_{IN \text{ AVERAGE}} \times 2.5V}{V_{OUT} \times \Delta V_{EAO} \times S \times C_{DC} \times 380V} \times G_m \times Z_C \quad (4)$$


$$\frac{1}{2\pi \times R_{fb} \times C_{fb}} > 150Hz$$

$$Ex: \frac{1}{2\pi \times 47k \times C_{fb}} > 150Hz$$

$$C_{fb} < 22nF$$


$C_{fb}$  可選用102或103

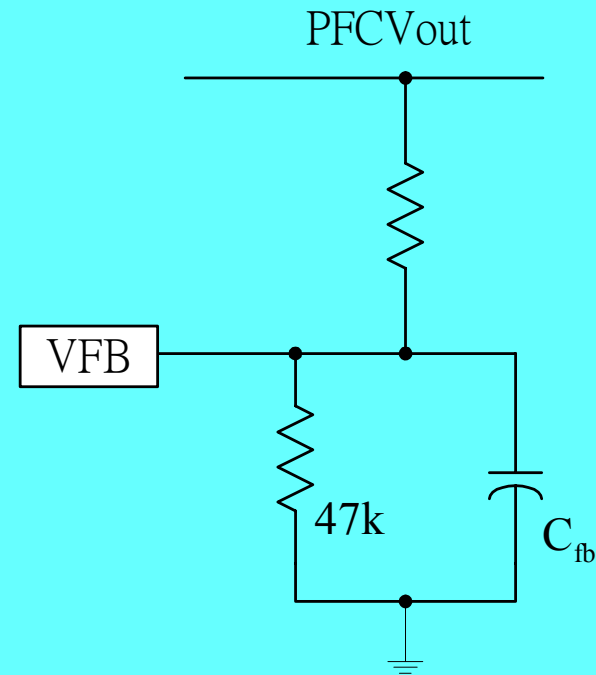

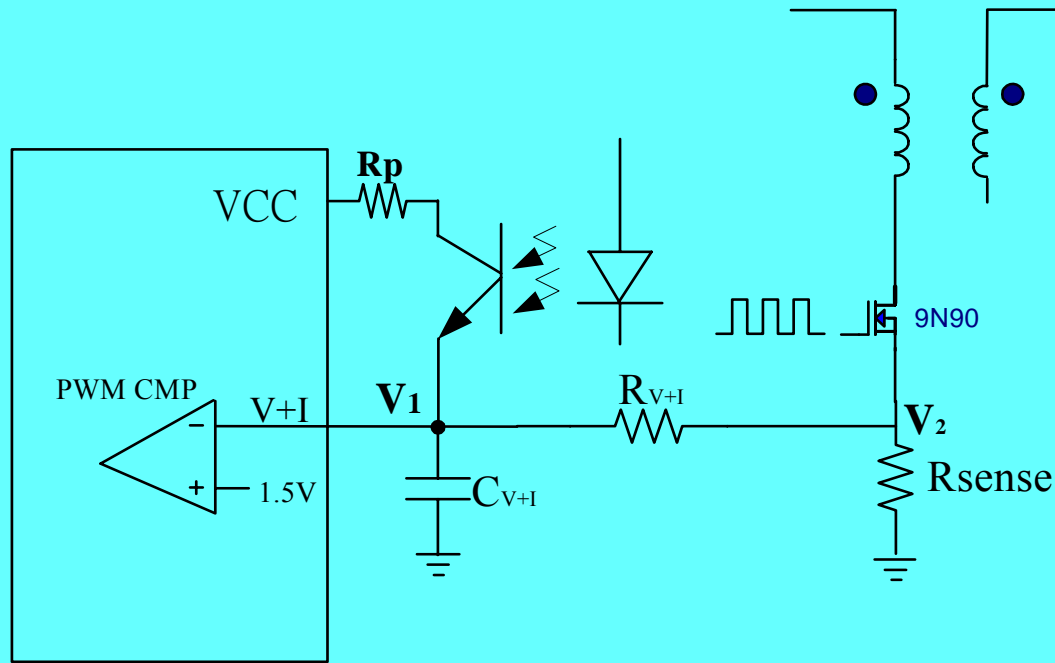

$$R_p = \frac{V_{CC} - V_{CE} - (V + I)}{\text{photo couple curret}} = \frac{15 - 1 - 1.5}{10\text{mA}} = 1.25\text{K}$$

# Championmicro

 

$$R_{V+I} = \frac{V_{1.5(V+I)} - V_{RsensePeak}}{\text{photo Couple Current(Full Load)}}$$

$$= \frac{1.5 - V_{RsensePeak}}{\text{Photo Couple Current(Full Load)}}$$




一般約取  $V_{RsensePeak}$  為  $1.25V$

$$= \frac{0.25}{\text{Photo Couple Current(Full Load)0.5mA}}$$



協助提升系統的暫態響應能力，一般而言，設計目標是讓控制迴路和45度相位邊限 (phase margin) ， $C_{V+I}$ 與 $R_{sense}$ 極點控制濾波在開關頻率內。
  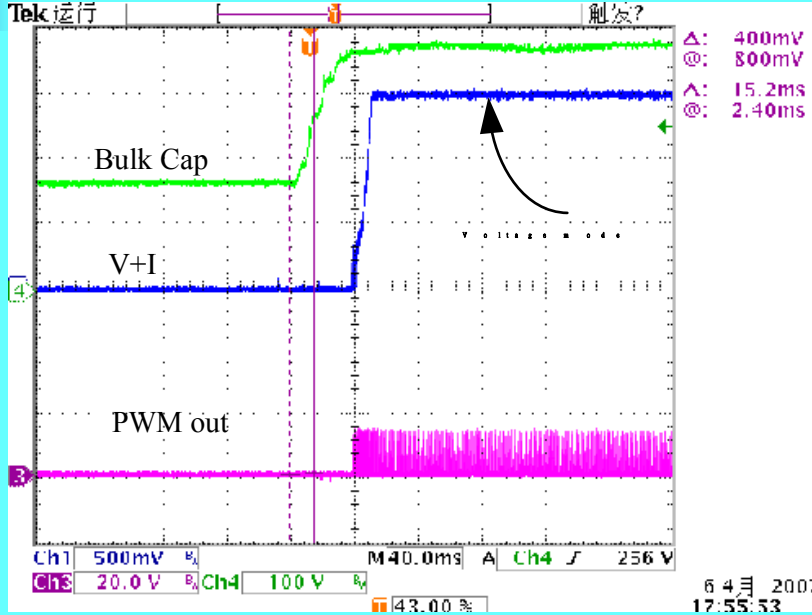
$$C_{V+I} = \frac{1}{2\pi R_{V+I} f_{sw}} = \frac{1}{2\pi 500 67 K} \approx 4700 PF$$










## PFC PWM timing

 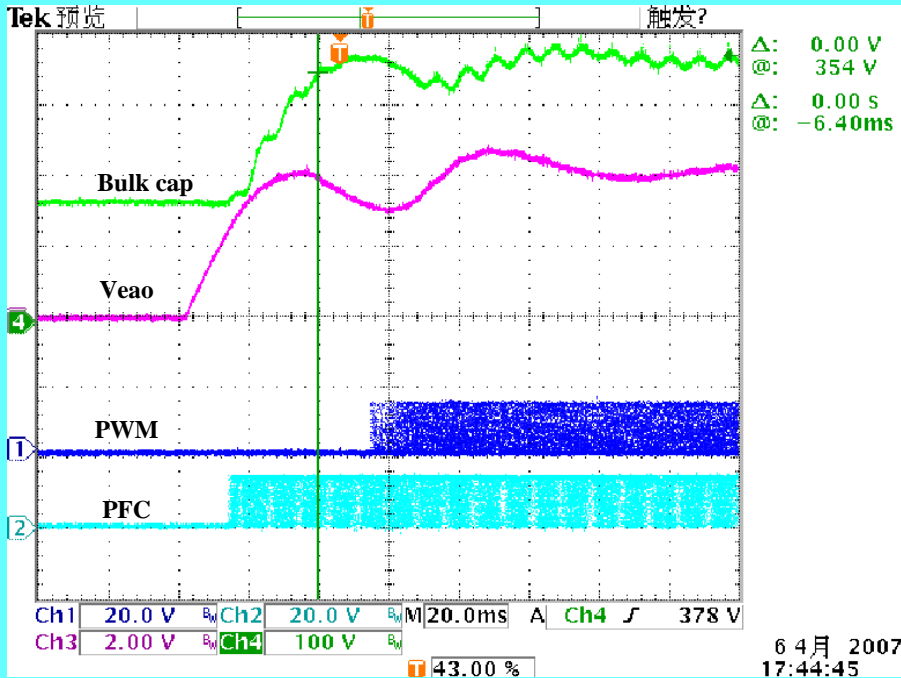

# Championmicro

  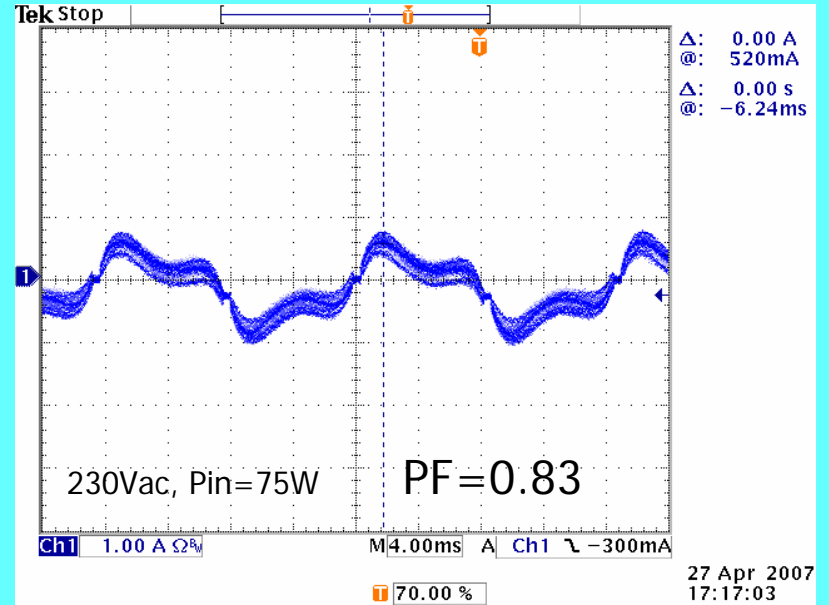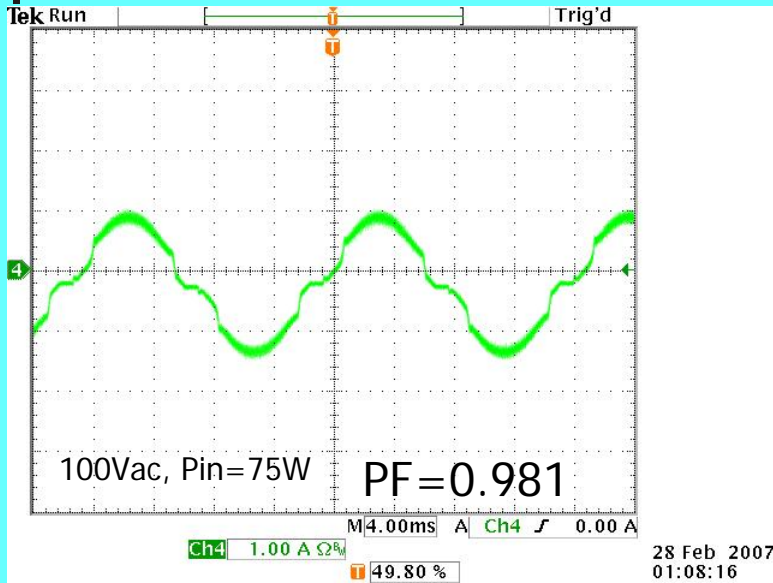

## Improve and Enhance THD

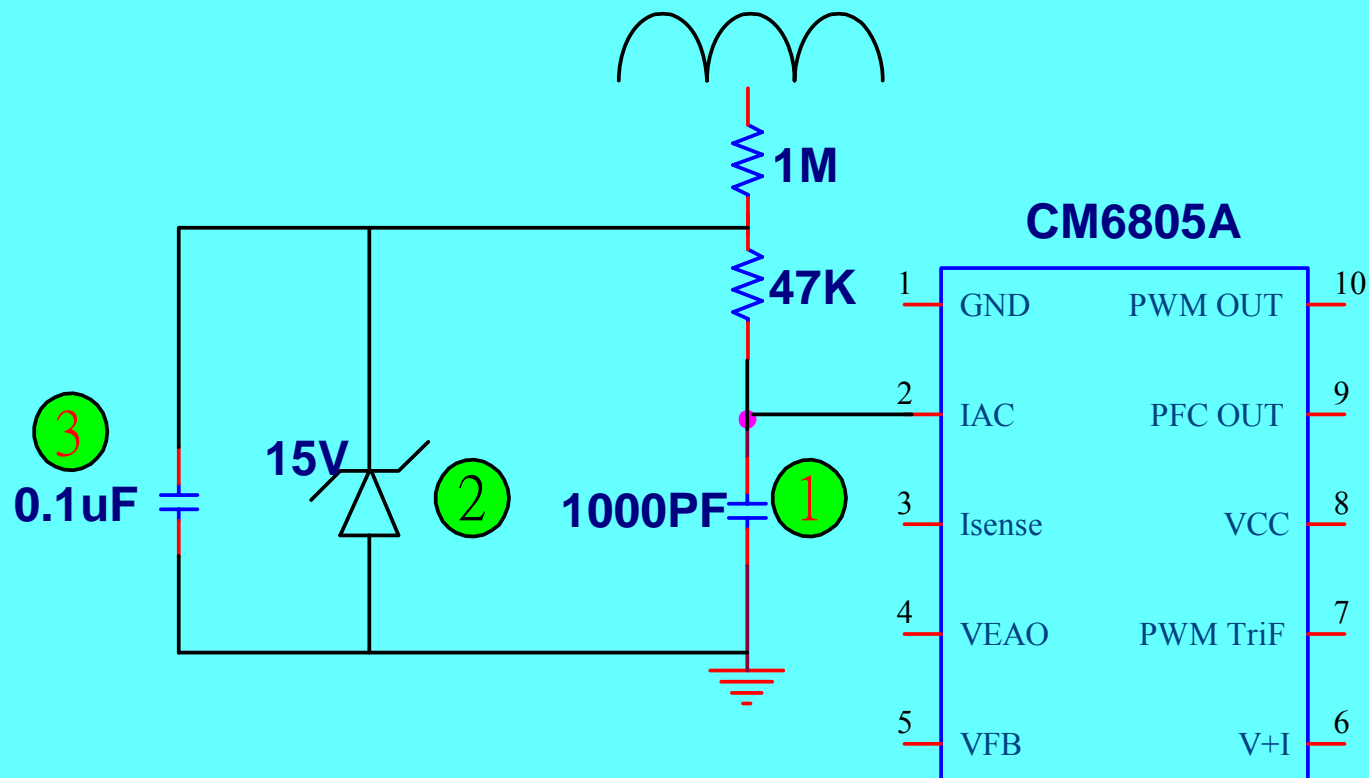

# Disable PWM skipping

