



## **To Calculate Average and Peak Pulse Current Working in PFC Diode**

**Jason Hsu 許元豪, Sr. Application Engineer**

# 1. To Calculate Average Current of PFC Diode


**Step 1.** 
$$I_{in\_RMS} = \frac{P_{out}}{V_{in\_min} \cdot \eta}$$

**Step 2.** 
$$D_{on, avg. (FET)} = 1 - ( V_{in\_min} / V_{out} )$$

**Step 3.** 
$$D_{on, avg. (Diode)} = 1 - D_{on, avg. (FET)}$$

**Step 4.** 
$$I_{avg. (Diode)} = I_{in\_RMS} * D_{on, avg. (Diode)}$$
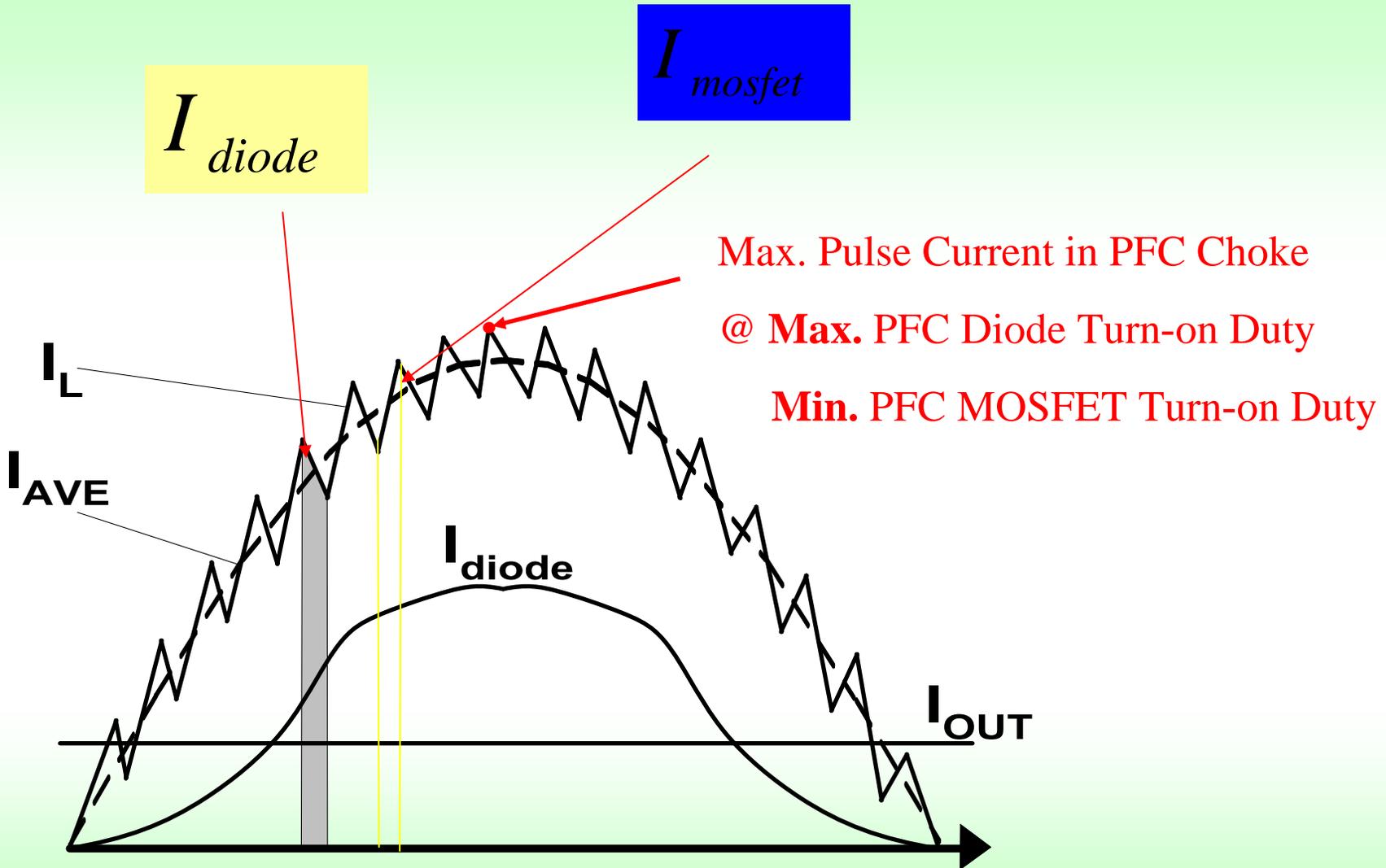
## 2. To Calculate Peak Repetitive Pulse Current of PFC Diode - (1)



## 2. To Calculate Peak Repetitive Pulse Current of PFC Diode - (2)

**Step 1.** 
$$I_{in\_RMS} = \frac{P_{out}}{V_{in\_min} \cdot \eta}$$

**Step 2.** 
$$I_{in\_pk} = \sqrt{2} \cdot I_{in\_RMS}$$

**Step 3.** high frequency current in PFC Choke, peak to peak,  
$$I_{HF} \approx 30\% * I_{in\_pk}$$

**Step 4.** 
$$I_{max. pulse (Diode)} = I_{in\_pk} + 1/2 * I_{HF}$$

**Step 5.** 
$$D_{on, min. (FET)} = 1 - (\sqrt{2} * V_{in\_min} / V_{out})$$

$$D_{on, max. (Diode)} = 1 - D_{on, min (FET)}$$



*Example #1 :*

**1KW PFC Application**

## Target Specification of 1KW PFC

Input voltage	<b>90VAC ~ 265VAC</b>
Input frequency	50Hz
Output voltage and current	<b>400VDC</b>
Output power	<b>1KW</b>
Efficiency	<b>&gt;92% at full load</b>
Switching Frequency	<b>70KHz</b>
Maximum Ambient temperature around PFC	<b>50°C</b>

# 1. To Calculate Average Current of PFC Diode

**Step 1.** 
$$I_{in\_RMS} = \frac{P_{out}}{V_{in\_min} \cdot \eta} = 1KW / (90 * 92\%) = 12.07A$$


**Step 2.** 
$$D_{on, avg. (FET)} = 1 - (V_{in\_min} / V_{out}) = 1 - (90 / 400) = 0.775$$

**Step 3.** 
$$D_{on, avg. (Diode)} = 1 - D_{on, avg. (FET)} = 1 - 0.775 = 0.225$$

**Step 4.** 
$$I_{avg. (Diode)} = I_{in\_RMS} * D_{on, avg. (Diode)} = 12.07 * 0.225 = \underline{\underline{2.72A}}$$



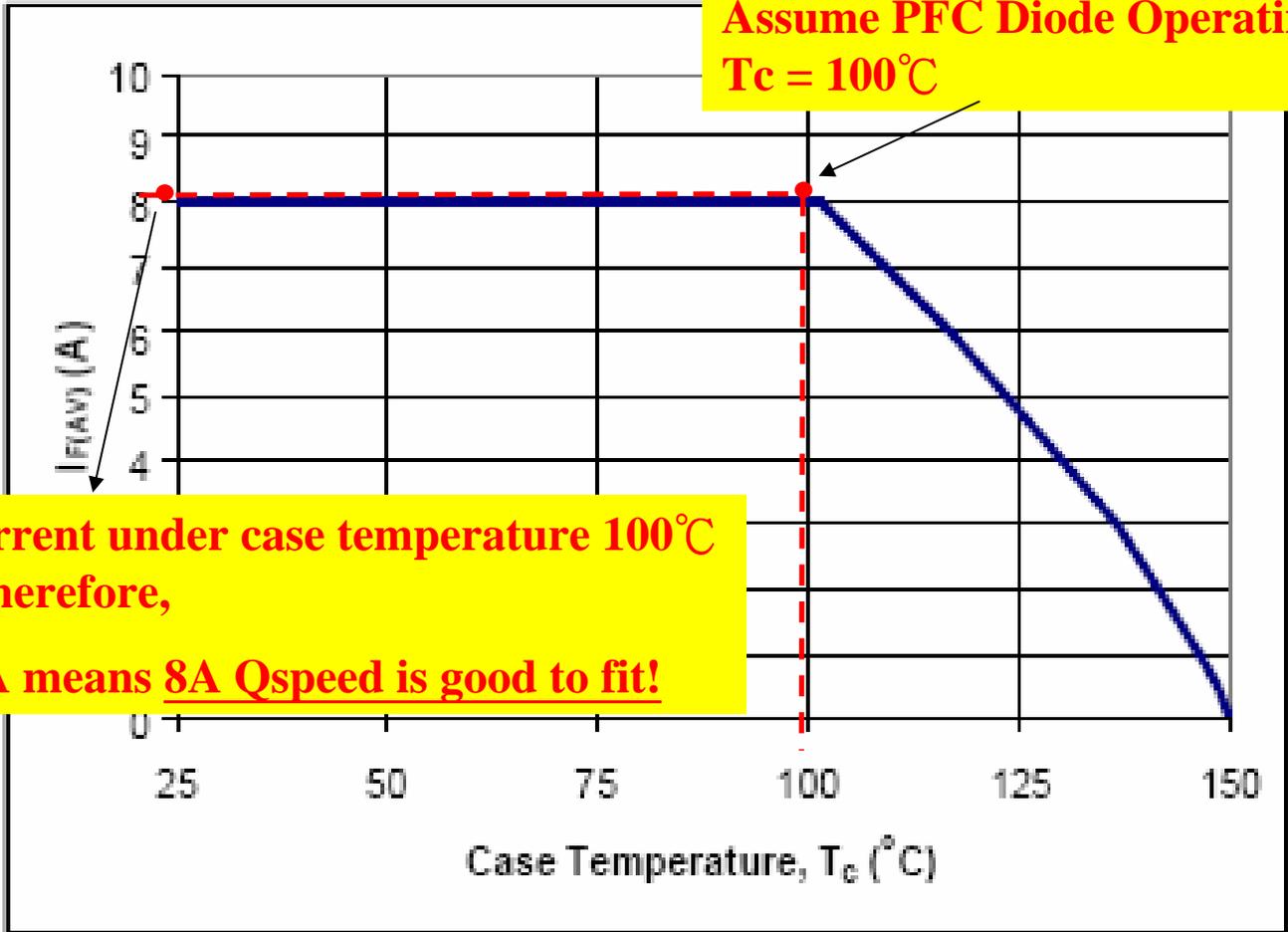**Assume PFC Diode Operating Condition :  
 $T_c = 100^\circ\text{C}$**



**The DC Current under case temperature  $100^\circ\text{C}$  is 8A, and therefore,  
 $8\text{A} \gg 2.72\text{A}$  means 8A Qspeed is good to fit!**

**LQA08TC600 DC Current Derating Curve**

## 2. To Calculate Peak Repetitive Pulse Current of PFC Diode

**Step 1.** 
$$I_{in\_RMS} = \frac{P_{out}}{V_{in\_min} \cdot \eta} = 1KW / (90 * 95\%) = 12.07A$$

**Step 2.** 
$$I_{in\_pk} = \sqrt{2} \cdot I_{in\_RMS} = 12.07 * 1.414 = 17.07A$$

**Step 3.** high frequency current in PFC Choke, peak to peak,


$$I_{HF} \approx 30\% * I_{in\_pk} = 17.07 * 30\% = 5.12A$$

**Step 4.** 
$$I_{max. pulse (Diode)} = I_{in\_pk} + 1/2 * I_{HF} = 17.07 + 0.5 * 5.12 = \underline{19.63A}$$

**Step 5.** 
$$D_{on, min. (FET)} = 1 - ( \sqrt{2} * V_{in\_min} / V_{out} )$$
$$= 1 - ( \sqrt{2} * 90 / 400 ) = 0.68$$

$$D_{on, max. (Diode)} = 1 - D_{on, min (FET)} = 1 - 0.68 = 0.32$$

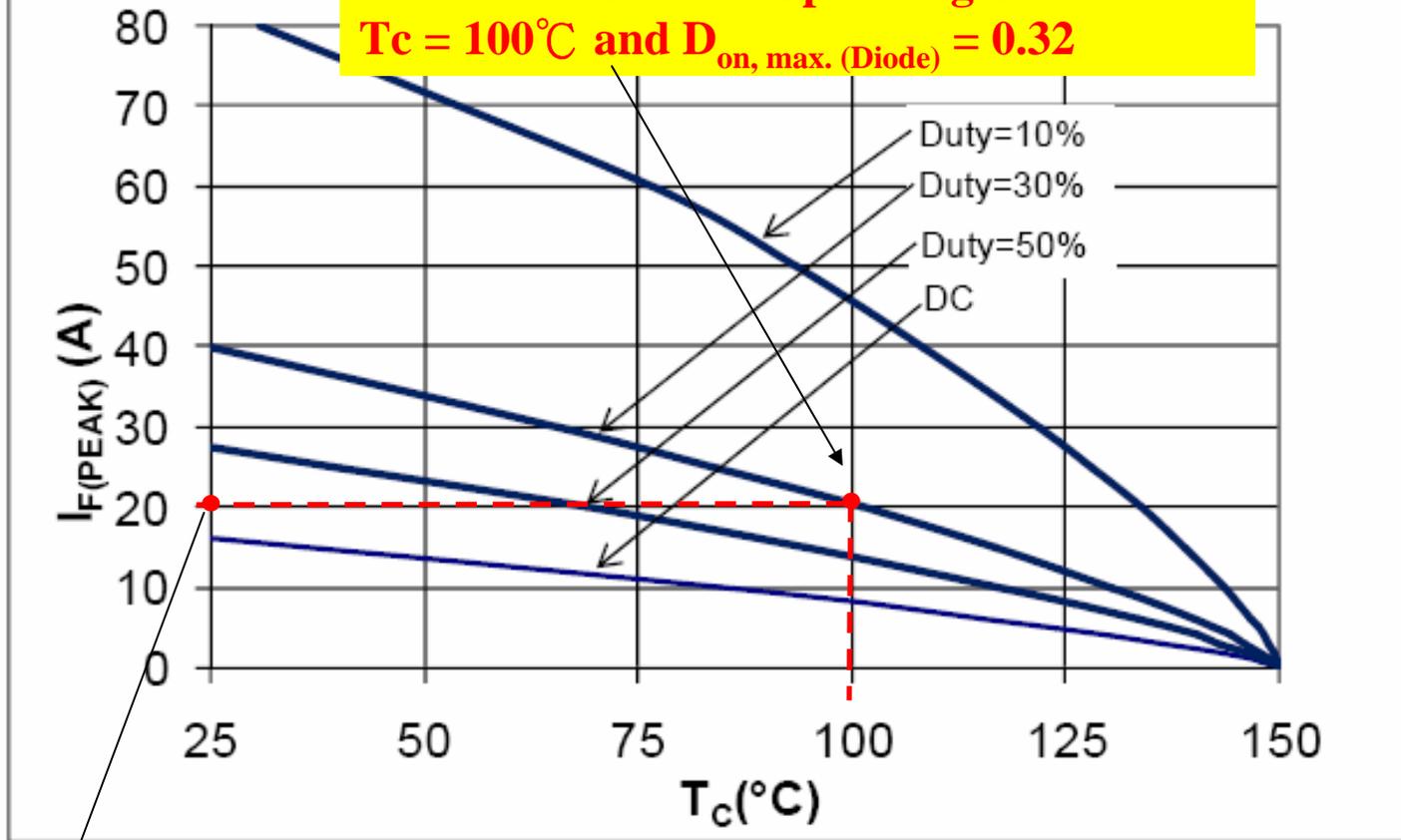Assume PFC Diode Operating Condition :  
 $T_c = 100^\circ\text{C}$  and  $D_{\text{on, max. (Diode)}} = 0.32$



LQA08TC600  $I_{F(\text{PEAK})}$  vs  $T_c$ ,  $f=70\text{kHz}$ .

The sustainable repetitive pulse current under this operation condition is 20.5A, and therefore,

**20.5A > 19.63A means 8A Qspeed is good to fit!**



*Example #2 :*

**500W PFC Application**

## Target Specification of 500W PFC

Input voltage	<b>90VAC ~ 265VAC</b>
Input frequency	50Hz
Output voltage and current	<b>400VDC</b>
Output power	<b>500W</b>
Efficiency	<b>&gt;92% at full load</b>
Switching Frequency	<b>70KHz</b>
Maximum Ambient temperature around PFC	<b>50°C</b>


# 1. To Calculate Average Current of PFC Diode

**Step 1.** 
$$I_{in\_RMS} = \frac{P_{out}}{V_{in\_min} \cdot \eta} = 500W / (90 * 92\%) = 6.04A$$

**Step 2.** 
$$D_{on, avg. (FET)} = 1 - (V_{in\_min} / V_{out}) = 1 - (90 / 400) = 0.775$$

**Step 3.** 
$$D_{on, avg. (Diode)} = 1 - D_{on, avg. (FET)} = 1 - 0.775 = 0.225$$

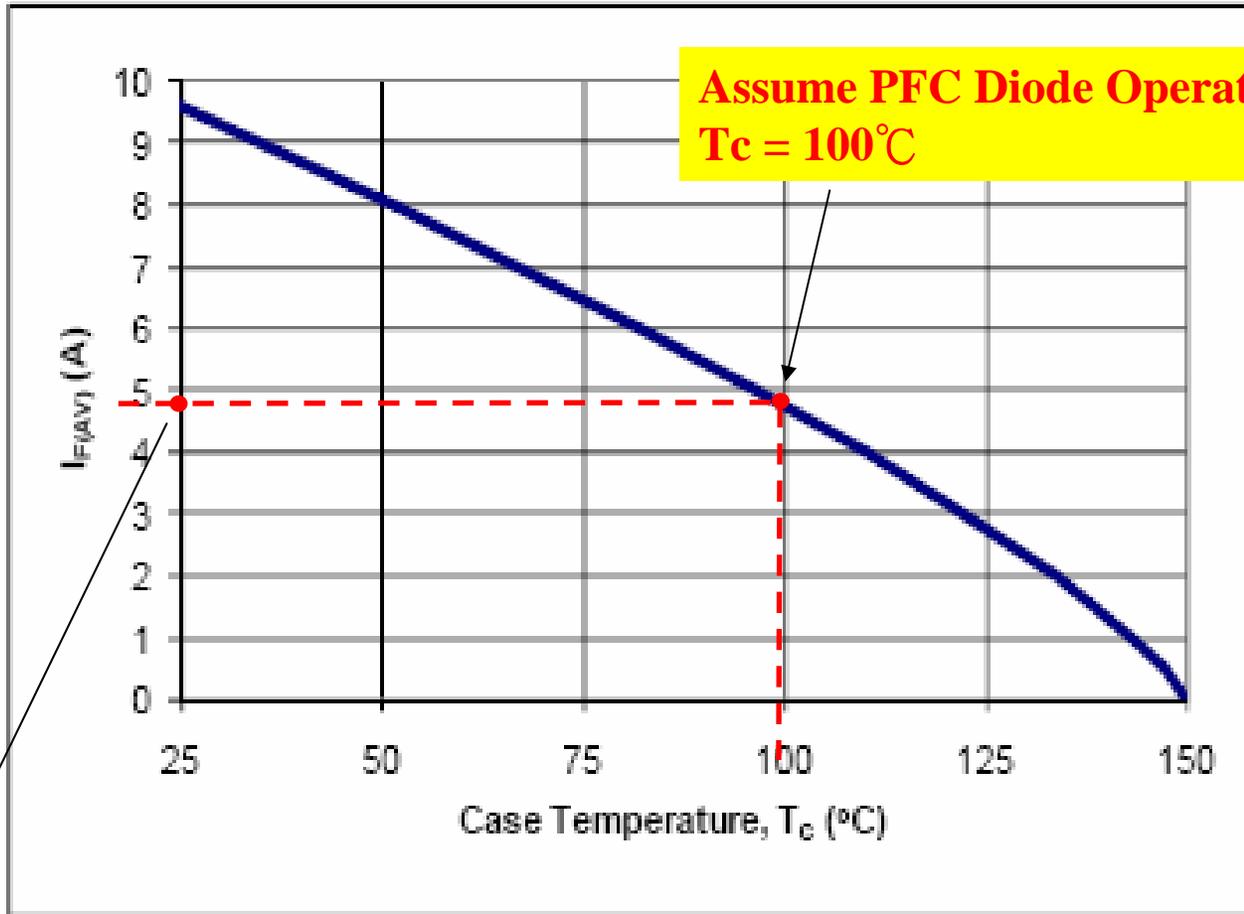**Step 4.** 
$$I_{avg. (Diode)} = I_{in\_RMS} * D_{on, avg. (Diode)} = 6.04 * 0.225 = \underline{\underline{1.36A}}$$



**LQA03TC600 DC Current Derating Curve**

The DC Current under case temperature  $100^{\circ}\text{C}$  is 4.7A, and therefore,

**4.7A  $\gg$  1.36A means 3A Qspeed is good to fit!**

## 2. To Calculate Peak Repetitive Pulse Current of PFC Diode

**Step 1.** 
$$I_{in\_RMS} = \frac{P_{out}}{V_{in\_min} \cdot \eta} = 500W / (90 * 95\%) = 6.04A$$

**Step 2.** 
$$I_{in\_pk} = \sqrt{2} \cdot I_{in\_RMS} = 6.04 * 1.414 = 8.54A$$

**Step 3.** high frequency current in PFC Choke, peak to peak,


$$I_{HF} \approx 30\% * I_{in\_pk} = 8.54 * 30\% = 2.56A$$

**Step 4.** 
$$I_{max. pulse (Diode)} = I_{in\_pk} + 1/2 * I_{HF} = 8.54 + 0.5 * 2.56 = \underline{9.82A}$$

**Step 5.** 
$$D_{on, min. (FET)} = 1 - (\sqrt{2} * V_{in\_min} / V_{out})$$
$$= 1 - (\sqrt{2} * 90 / 400) = 0.68$$

$$D_{on, max. (Diode)} = 1 - D_{on, min (FET)} = 1 - 0.68 = 0.32$$

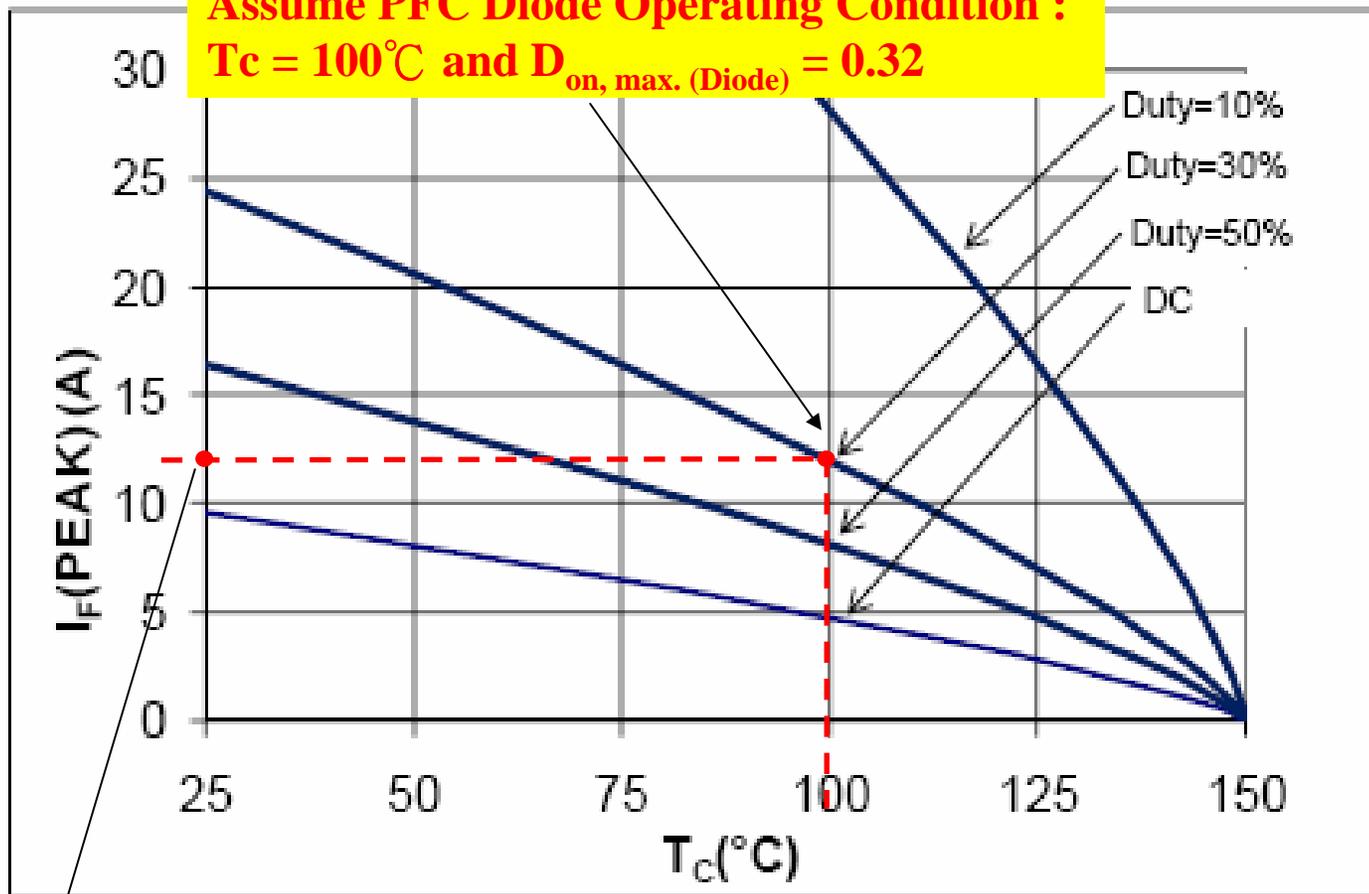**Assume PFC Diode Operating Condition :  
 $T_c = 100^\circ\text{C}$  and  $D_{\text{on, max. (Diode)}} = 0.32$**



**LQA03TC600  $I_F(\text{PEAK})$  vs  $T_c$ ,  $f=70\text{kHz}$ .**

**The sustainable repetitive pulse current under this operation condition is 12.5A, and therefore,**

**12.5A > 9.82A means 3A Qspeed is good to fit!**



*Take Action Now# :*

**According to Two Parameters Guaranteed by LQA03TC600,**

**Average DC Current and, Peak Repetitive Pulse Current,**

**3A Qspeed Can Be Safely Designed in 500W PFC Application**